


Summary of NMOS FET Mathematical Model Expressions

$$K_n = \mu_n C_{ox} \frac{W}{L}, \quad i_G = 0, \quad i_B = 0$$

Cut-off Region - $i_{DS} = 0$ for $v_{GS} \leq V_{TN}$

Linear region - $v_{GS} - V_{TN} \geq v_{DS} \geq 0$

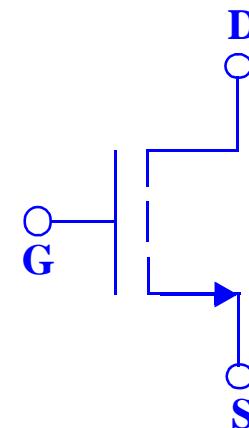
$$i_{DS} = K_n \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS}$$




Saturation region

$$v_{DS} \geq v_{GS} - V_{TN} \geq 0$$
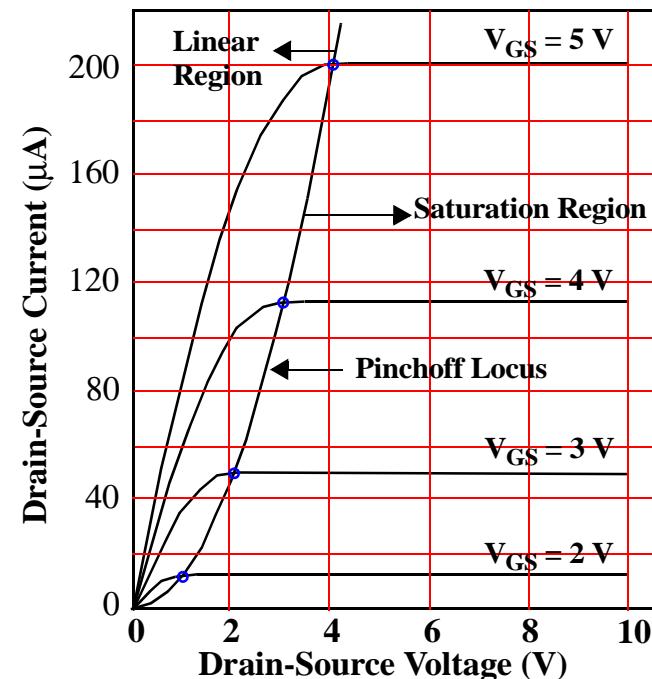
$$i_{DS} = \frac{K_n}{2} \frac{W}{L} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$



Body-Effect or Substrate Sensitivity

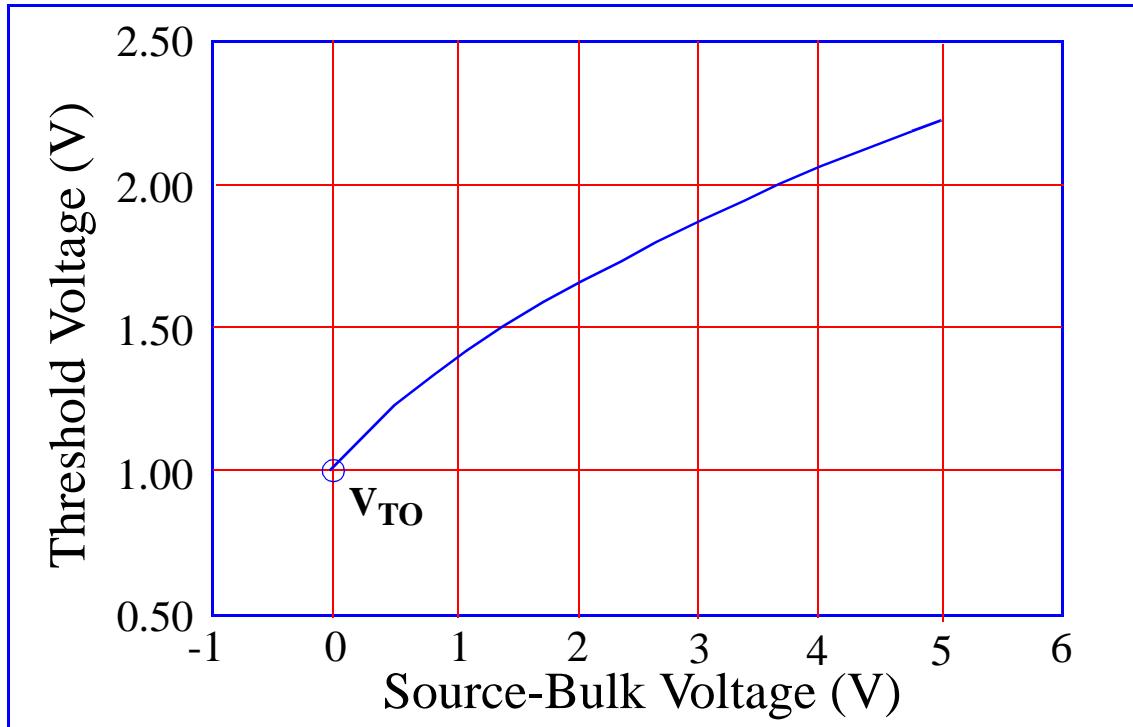

Threshold Voltage is

$$V_{TN} = V_{T0} + \gamma(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F})$$

V_{T0} = zero substrate bias value of V_{TN}

γ = body effect parameter ($V^{0.5}$)

$2\phi_F$ = surface potential parameter

Enhancement mode NMOSFETs $V_{TN} > 0$

Depletion mode NMOSFETs $V_{TN} \leq 0$

Example: Given an NMOS transistor with $V_{T0} = 1V$, $\phi_F = 0.3V$, $\gamma = 0.7\sqrt{V}$, find V_{TN} for $v_{SB} = 0, 1, 2, 3, 4$ and 5 V respectively. (Ans. = $1, 1.34, 1.59, 1.79, 1.96$ and 2.11 V respectively.)

Use $V_{TN} = V_{T0} + \gamma(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F})$:


for $v_{SB} = 1$ V,

$$V_{TN} = V_{T0} + \gamma(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F}) = 1 + 0.7(\sqrt{1 + 2 \times 0.3} - \sqrt{2 \times 0.3}) = 1.34V$$

for $v_{SB} = 4$ V,

$$V_{TN} = V_{T0} + \gamma(\sqrt{v_{SB} + 2\phi_F} - \sqrt{2\phi_F}) = 1 + 0.7(\sqrt{4 + 2 \times 0.3} - \sqrt{2 \times 0.3}) = 1.96V$$

PMOS FET

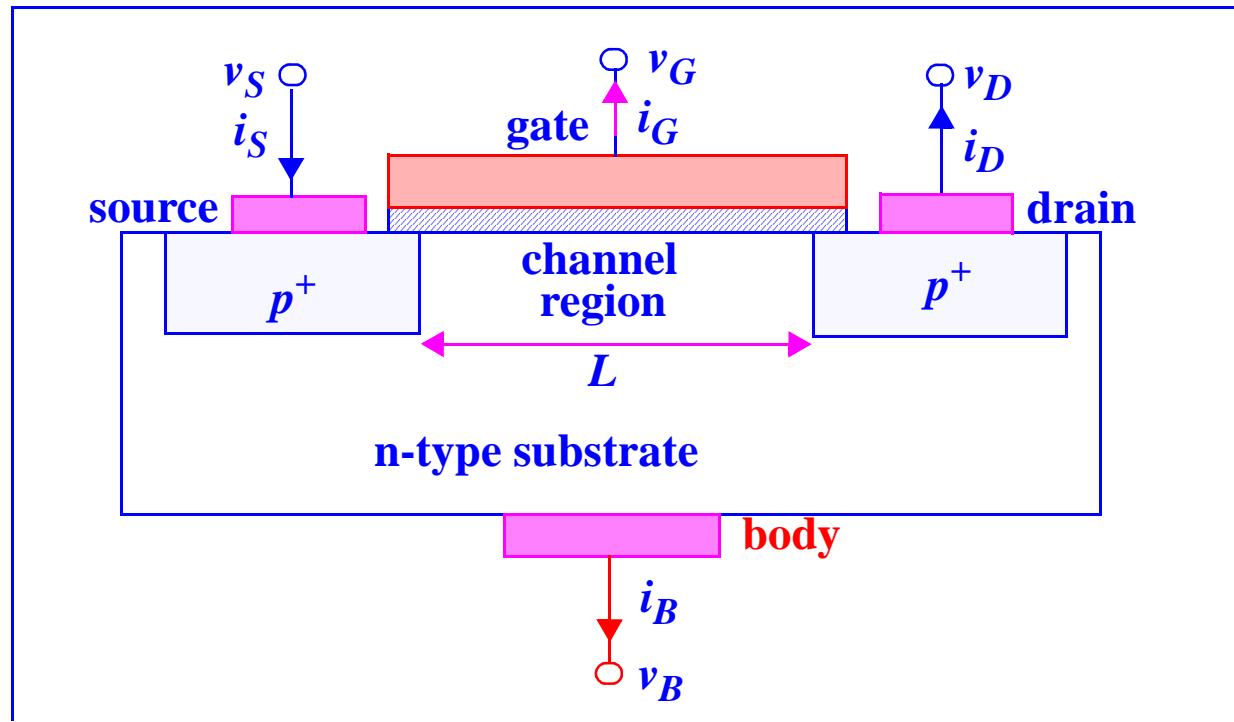

To Obtain an inversion layer throughout the channel we must have

$$G - v_c \leq V_{Tp} \Rightarrow -v_G \geq -v_c - V_{Tp} \Rightarrow v_s - v_G \geq v_s - v_c - V_{Tp}$$

$$v_{SG} + V_{TP} \geq v_{SD}$$

Summary of PMOS FET Mathematical Model Expressions

$$K_p = \mu_p C_{ox} \frac{W}{L}, \quad i_G = 0, \quad i_B = 0$$

Cut-off Region - $i_{SD} = 0$ for $v_{SG} \leq -V_{TP}$ or $v_{GS} \geq V_{TP}$

Linear region - $v_{SG} + V_{TP} \geq v_{SD} \geq 0$

$$i_{SD} = K_p \left(v_{SG} + V_{TP} - \frac{v_{SD}}{2} \right) v_{SD}$$

Saturation region - $v_{SD} \geq v_{SG} + V_{TP} \geq 0$


$$i_{SD} = \frac{K_p}{2} (v_{SG} + V_{TP})^2 (1 + \lambda v_{SD})$$

Threshold Voltage is $V_{TP} = V_{T0} - \gamma (\sqrt{v_{BS} + 2\phi_F} - \sqrt{2\phi_F})$


Enhancement mode PMOSFETs $V_{TP} < 0$

Depletion mode PMOSFETs $V_{TP} \geq 0$

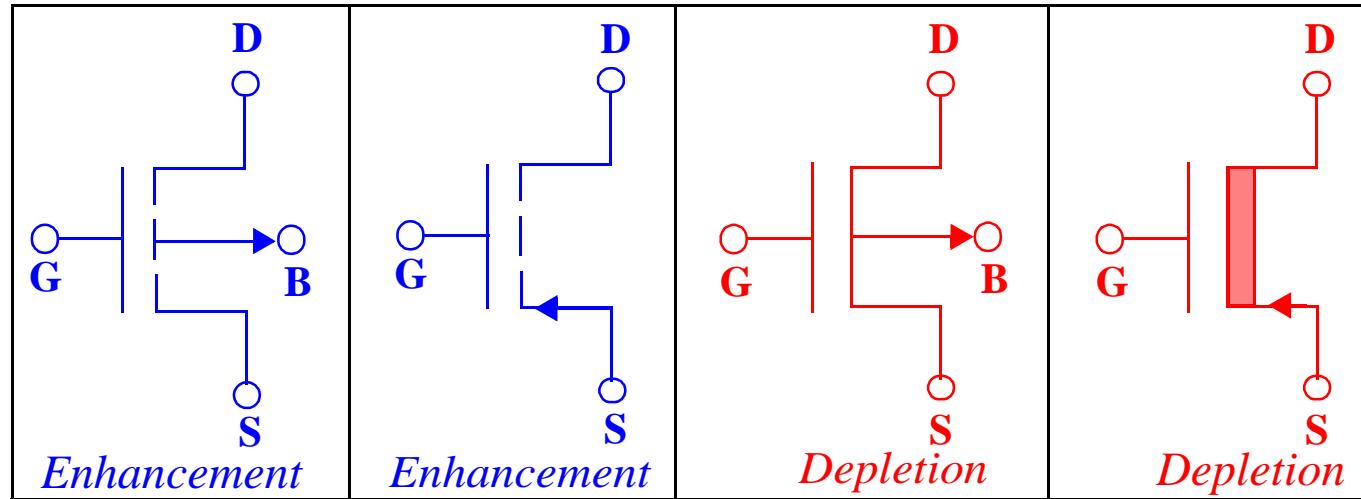Symbols of the p-channel MOS Transistor or PMOSFET



Biasing the MOSFET

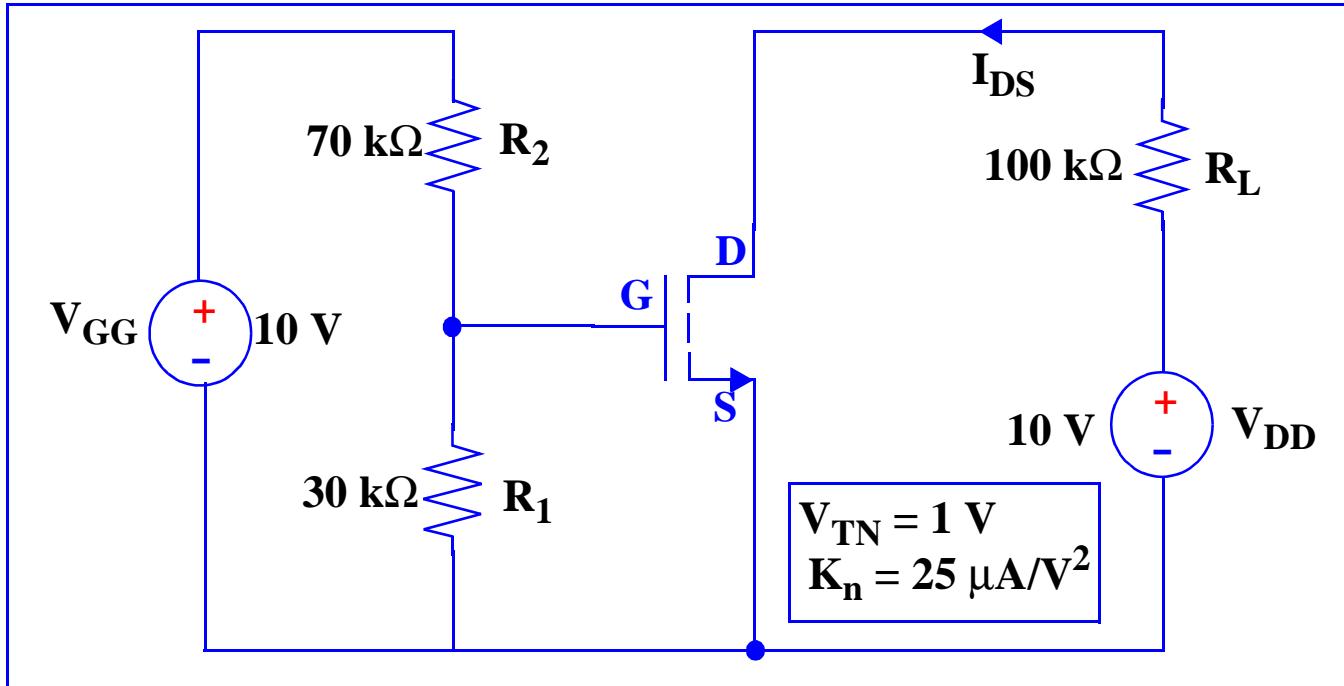

$$V_G = \frac{30\text{ k}\Omega}{30\text{ k}\Omega + 70\text{ k}\Omega} 10\text{ V} = 3\text{ V} \text{ and } V_S = 0\text{ V}. \therefore V_{GS} = 3\text{ V}$$

Assume MOSFET is in saturation mode, so the drain current is

$$I_{DS} = \frac{K_n}{2}(V_{GS} - V_{TN})^2 = \frac{25}{2}(3 - 1)^2 = 50\text{ }\mu\text{A}.$$

$$V_{DS} = V_{DD} - I_{DS} R_L = 10\text{ V} - 50\text{ }\mu\text{A} \cdot 100\text{ k}\Omega = 5\text{ V}.$$

$$\text{But } V_{GS} - V_{TN} = 3\text{ V} - 1\text{ V} = 2\text{ V} \Rightarrow V_{DS} > V_{GS} - V_{TN}.$$

Therefore, our assumption of the operating mode of the MOS transistor is correct.

The Q-Point of the MOSFET is $I_{DS}, V_{DS}, V_{GS} = 50\mu A, 5V, 3V$.

For load-line - $V_{DD} = I_{DS}R_L + V_{DS}$ or $10 = 10^5I_{DS} + V_{DS}$

