

# Lecture 19: Introduction to Small Signal Analysis

## From Chapter 13 in Jaeger, Chapter 8 in Spencer

### Outline/objective

Understanding the essence of SS modeling

Developing SS model of a diode

Illustration of utilizing SS model of a diode through an example

Suggested problems: 13.16, 13.43, 13.66, 13.101, 13.102

## Some Notations

$V_D$  dc voltage across the diode

$I_D$  dc current through the diode where

$$I_D = I_S (\exp(V_D / V_T) - 1)$$

$v_d(t)$  small signal voltage across the diode

$i_d(t)$  small signal current through the diode

$v_D$  total voltage across the diode where

$$v_D = V_D + v_d(t)$$

$i_D$  total current through the diode where


$$i_D = I_D + i_d(t)$$

the total voltage and total current are related by

$$I_D + i_d(t) = I_s (\exp((V_D + v_d(t))/V_T) - 1)$$

our target is to relate  $i_d(t)$  and  $v_d(t)$  through a linear model

### Derivation of SS model for the diode

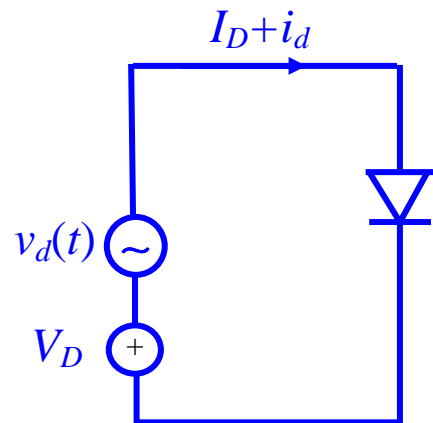

$$I_D + i_d(t) = I_s (\exp((V_D + v_d(t))/V_T) - 1)$$

$$I_D + i_d(t) = I_s (\exp(V_D/V_T) \exp(v_d(t)/V_T) - 1)$$

for very small values  $v_d \ll V_T$  we have

$$I_D + i_d(t) = I_s (\exp(V_D / V_T) [1 + (v_d / V_T)] - 1)$$

it follows that we have

$$i_d(t) = I_s \exp(V_D / V_T) (v_d / V_T)$$


but as  $I_s \exp(V_D / V_T) = I_D + I_s$  we get the final result

$$i_d(t) = ((I_D + I_s) / V_T) v_d(t) = g_d v_d(t)$$

small signal variations in the current are related to small signal variations of the voltage through the small signal conductance
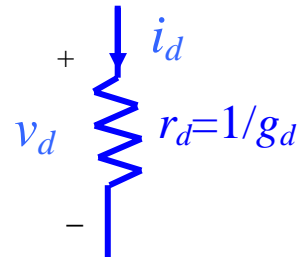
## SS Model of the diode

SS model of a diode is a resistor whose value depends on the dc bias conditions




Superposition allows us to separate the dc analysis and SS analysis

Two separate analyses may be carried out: a dc analysis to obtain the operating point and a SS analysis whose parameters are determined from the dc analysis

Remember that the total current and voltages are the sum of the dc and SS values
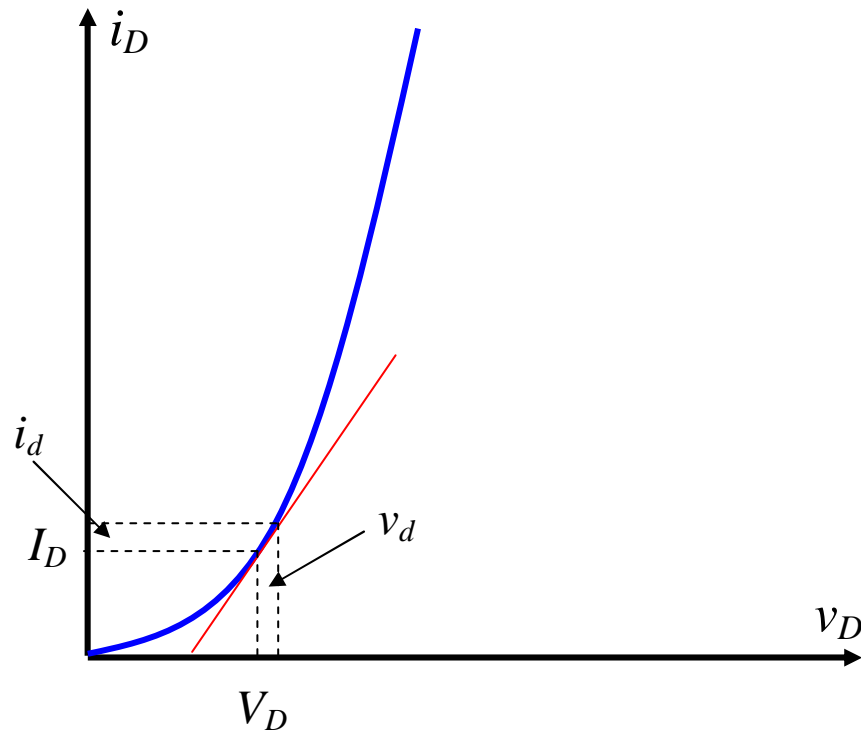
## Graphical Interpretation of the SS model of the Diode




$$g_d = \left. \frac{\partial i_D}{\partial v_D} \right|_{Q\text{-point}} = \left. \frac{\partial}{\partial v_d} \left\{ I_s \left[ \exp\left( \frac{v_D}{v_T} \right) - 1 \right] \right\} \right|_{Q\text{-Point}}$$

$$g_d = \frac{I_s}{V_T} \exp\left( \frac{V_D}{V_T} \right) = \frac{I_D + I_s}{V_T}$$

## General Procedure for SS analysis of any device

1. Carry out a dc analysis of the circuit. Determine the operating point of the device
2. Determine the values of the parameters of the small signal model
3. Replace the device by its small signal model to determine the small signal gain, input resistance, output resistance, etc.

## The Current-Controlled Attenuator

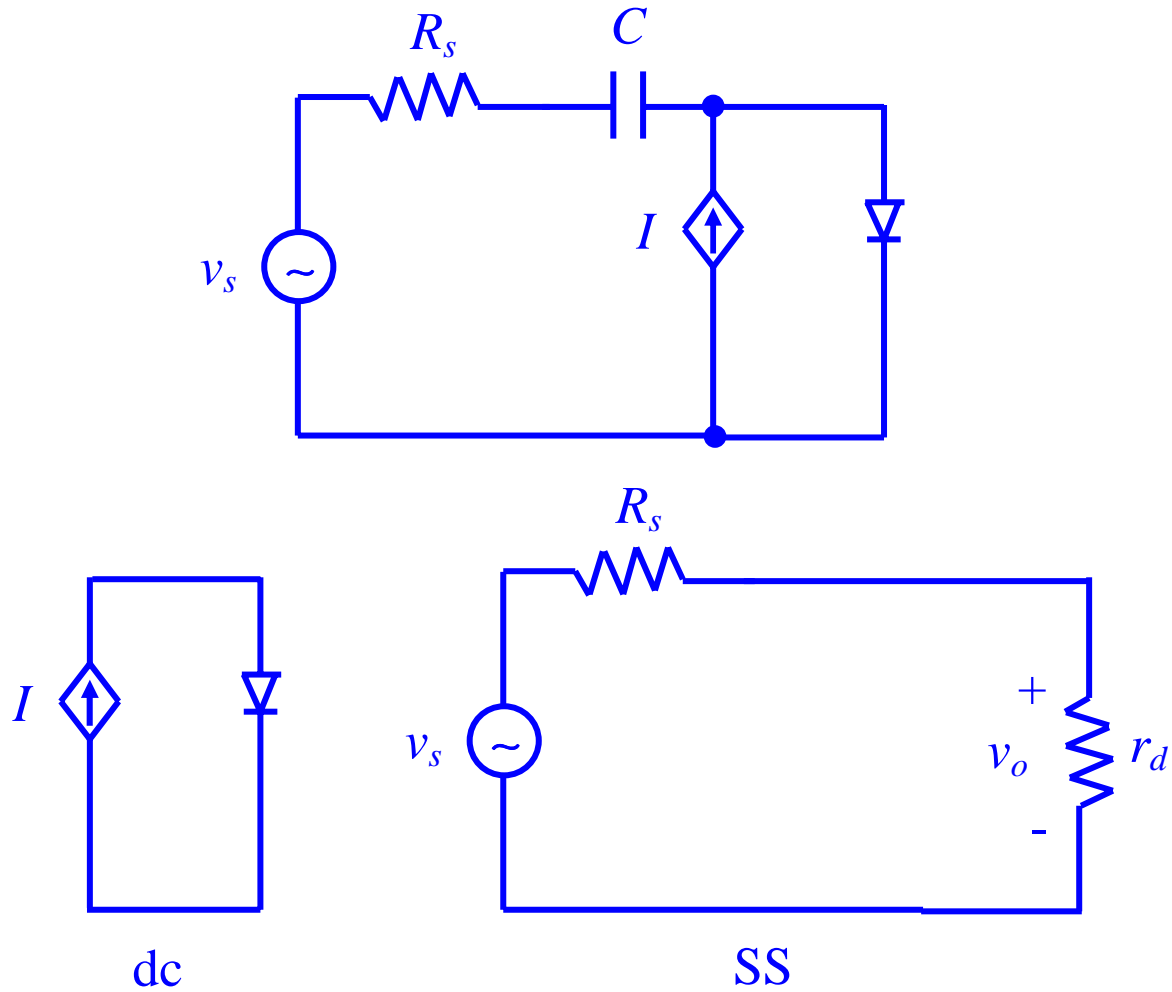



Using dc analysis  $I_D = I \Rightarrow g_d = (I_D + I_S) / V_T = 1 / r_d$

$$v_o = v_s (r_d / (r_d + R_s))$$

for  $R_s = 1.0 \text{K}\Omega$  and  $I_S = 1.0 \text{e-}5 \text{ A}$  we have

I	$r_d$	$v_o$
0	$25 \times 10^{12} \Omega$	$v_s$
$1 \mu\text{A}$	$25 \text{K}\Omega$	$0.96 v_s$
$10 \mu\text{A}$	$2.5 \text{K}\Omega$	$0.71 v_s$
$100 \mu\text{A}$	$250 \Omega$	$0.20 v_s$
$1.0 \text{mA}$	$25 \Omega$	$0.024 v_s$