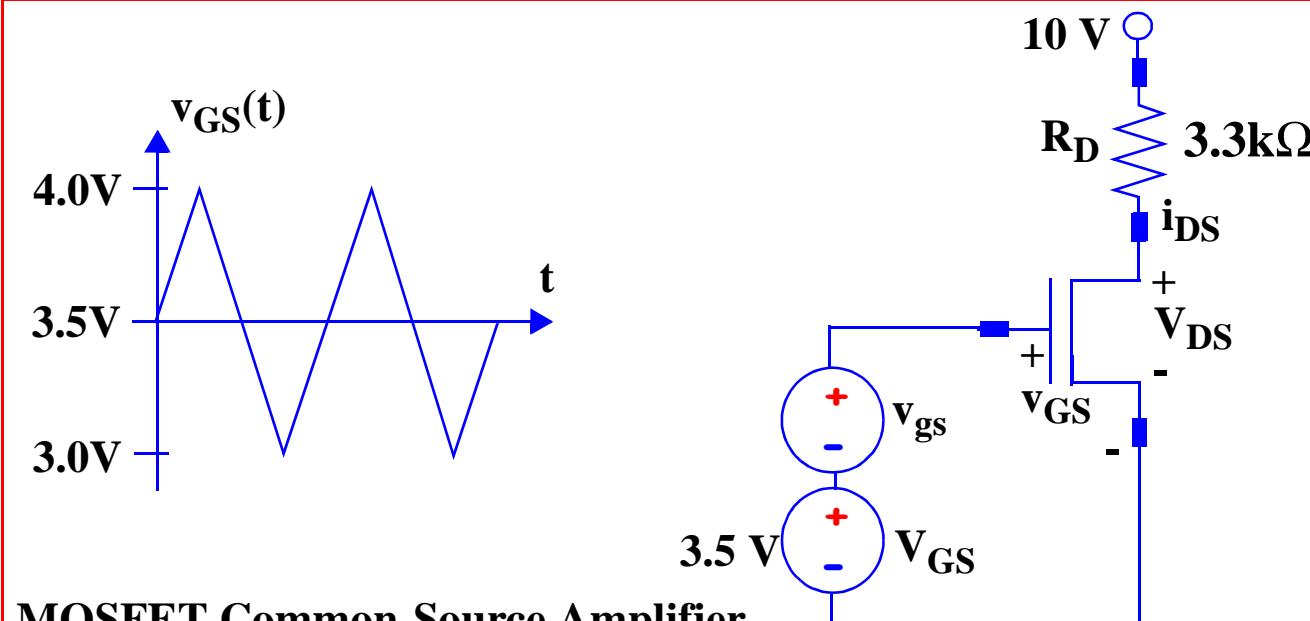



Lecture #20

Small-Signal Modeling & Linear Amplification - FETs

Outline/Learning Objectives:

- Describe the FET as an amplifier
- Define and describe the use of coupling and bypass capacitors
- Define and describe the small-signal model for the pn junction diode.
- Analyze FET amplifiers using a two-part process:
 - (1) dc Analysis:
 - (a) construct the dc equivalent circuit;
 - (b) solve for the Q-point.
 - (2) ac Analysis:
 - (3) construct the ac equivalent circuit;
 - (4) replace the FET by its small-signal model;
 - (5) solve the ac circuit.
- Define and describe the small-signal-model of the FET.
- Analyze the FET common-source (C-S) amplifier.
- Use the electronics laboratory to investigate the electrical behavior of simple circuits and devices.



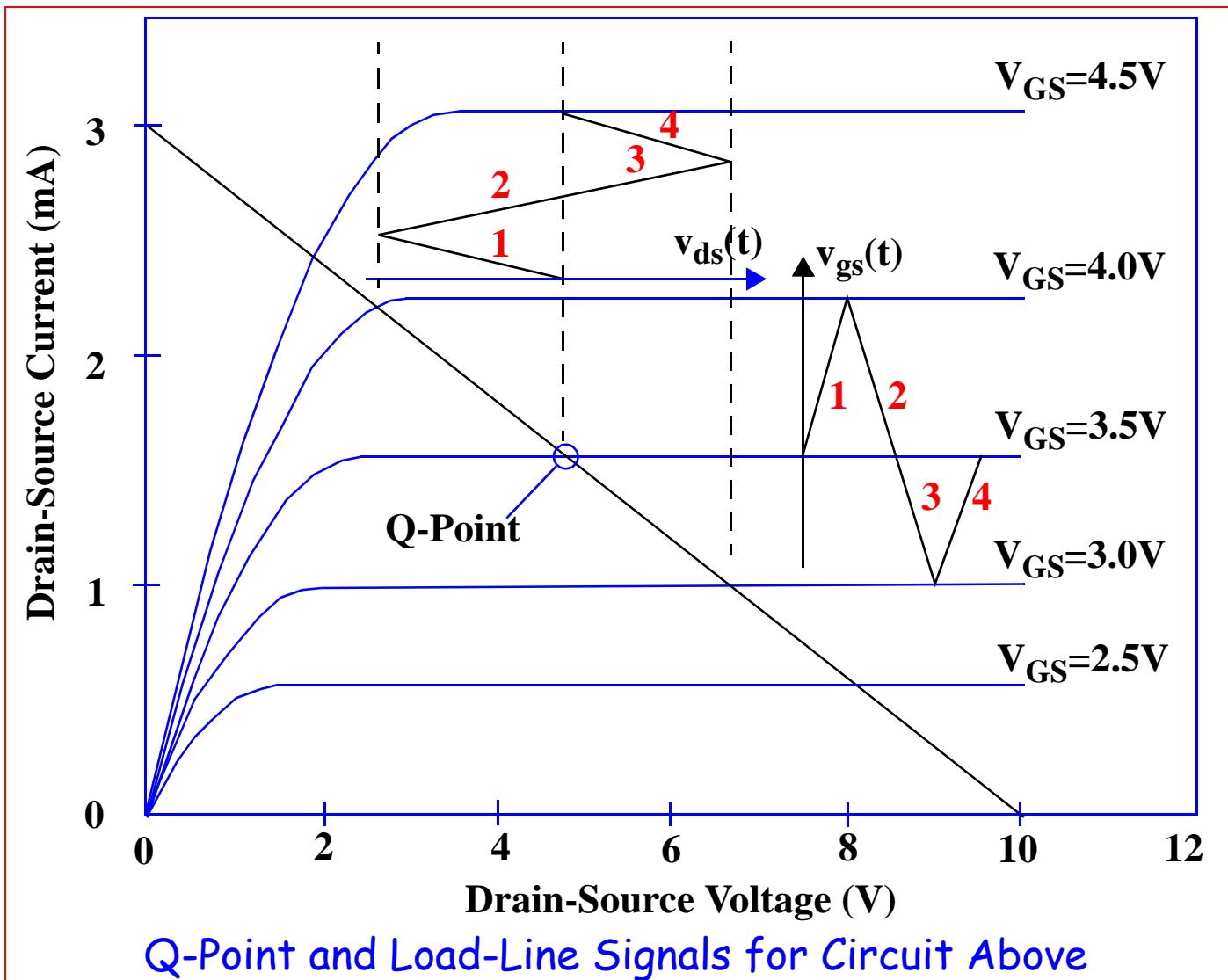

Small Signal Model of MOSFET


$$i_g = y_{11}v_{gs} + y_{12}v_{ds}$$

$$i_{ds} = y_{21}v_{gs} + y_{22}v_{ds}$$

$$v_{DS} = V_{DS} + v_{ds}; v_{GS} = V_{GS} + v_{gs}$$

$$i_G = I_G + i_g; i_{DS} = I_{DS} + i_{ds};$$
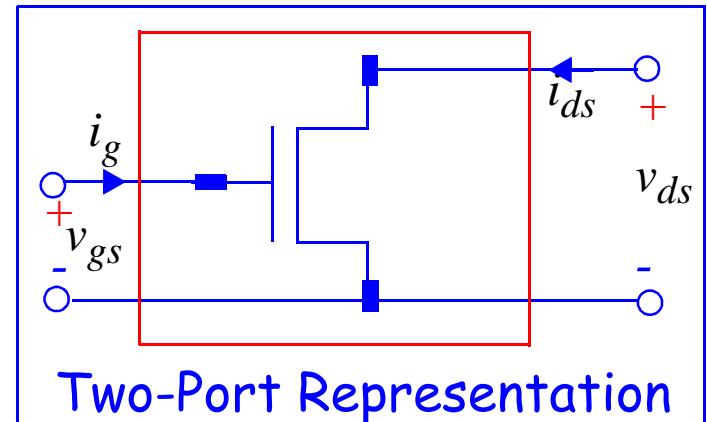
$$v_{gs} = \Delta v_{GS}, v_{ds} = \Delta v_{DS}, i_g = \Delta i_G \text{ and } i_{ds} = \Delta i_{DS}.$$



$$y_{11} = \left. \frac{i_g}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\partial i_G}{\partial v_{GS}} \right|_{Q-Point}$$

$$y_{12} = \left. \frac{i_g}{v_{ds}} \right|_{v_{gs}=0} = \left. \frac{\partial i_G}{\partial v_{DS}} \right|_{Q-Point}$$

$$y_{21} = \left. \frac{i_{ds}}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\partial i_{DS}}{\partial v_{GS}} \right|_{Q-Point}$$

$$y_{22} = \left. \frac{i_{ds}}{v_{ds}} \right|_{v_{gs}=0} = \left. \frac{\partial i_{DS}}{\partial v_{DS}} \right|_{Q-Point}$$


$$i_{DS} = \frac{K_n}{2}(v_{GS} - V_{TN})^2(1 + \lambda v_{DS})$$

with $K_n = \mu C_{ox} \frac{W}{L}$, $v_{DS} \geq (v_{GS} - V_{TN}) \geq 0$ and $i_G = 0$.

$$y_{11} = 0 \quad \text{and} \quad y_{12} = 0$$

$$y_{21} = K_n(V_{GS} - V_{TN})(1 + \lambda V_{DS}) = \frac{2I_{DS}}{V_{GS} - V_{TN}} = g_m$$
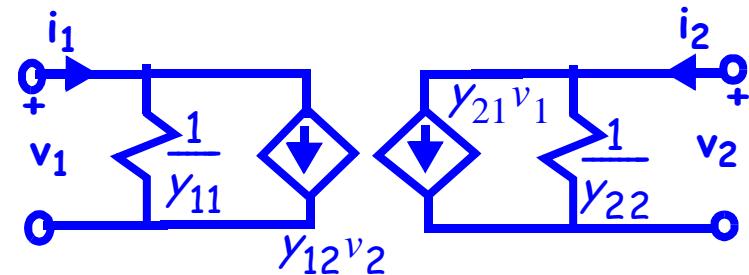
$$y_{22} = \frac{\lambda K_n}{2}(V_{GS} - V_{TN})^2 = \frac{\lambda I_{DS}}{1 + \lambda V_{DS}} = \frac{1}{r_o}$$




$$g_m = K_n(V_{GS} - V_{TN})(1 + \lambda V_{DS})$$

$$g_m = \sqrt{2K_n I_{DS}(1 + \lambda V_{DS})}.$$

$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}}.$$

For $\lambda V_{DS} \ll 1$,
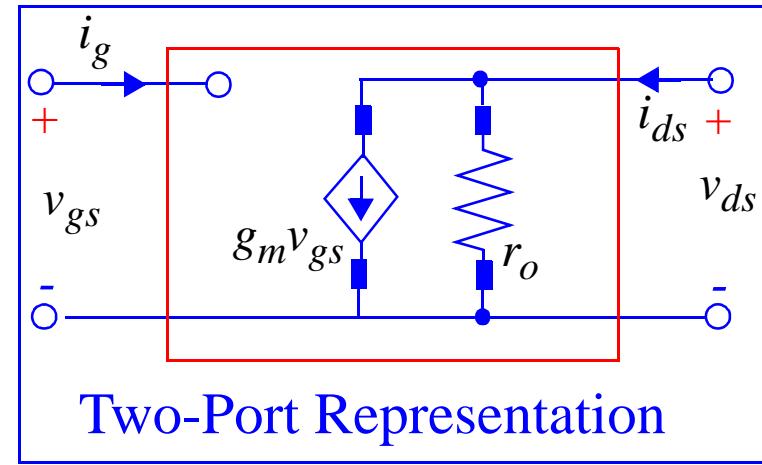
$$g_m = K_n(V_{GS} - V_{TN}) \quad \text{or} \quad g_m = \sqrt{2K_n I_{DS}}$$



Amplification Factor (μ_f)

$$\mu_f = g_m r_o = \frac{2I_{DS}}{V_{GS} - V_{TN}} \cdot \frac{1 + \lambda V_{DS}}{\lambda I_{DS}} = \frac{2(1 + \lambda V_{DS})}{\lambda(V_{GS} - V_{TN})}$$

$$\mu_f = g_m r_o = \sqrt{2K_n I_{DS}(1 + \lambda V_{DS})} \cdot \frac{1 + \lambda V_{DS}}{\lambda I_{DS}}$$

$$\mu_f = g_m r_o = \left(\frac{1}{\lambda} + V_{DS}\right) \cdot \sqrt{\frac{2K_n}{I_{DS}}(1 + \lambda V_{DS})}$$

For $\lambda V_{DS} \ll 1$,

$$\mu_f \approx \frac{1}{\lambda} \cdot \sqrt{\frac{2K_n}{I_{DS}}} \approx \frac{2}{\lambda(V_{GS} - V_{TN})}$$

I_D	g_m	r_o	μ_f
1 μ A	4.76×10^{-5} S	85.20 M Ω	4060
10 μ A	1.51×10^{-4} S	8.52 M Ω	1280
100 μ A	4.76×10^{-4} S	852 k Ω	406
1 mA	1.51×10^{-3} S	85.2 k Ω	128
10 mA	4.76×10^{-3} S	8.52 k Ω	40

Definition of Small-Signal Operation of MOSFET

$$i_{DS} = \frac{K_n}{2}(v_{GS} - V_{TN})^2 \text{ for } v_{DS} \geq (v_{GS} - V_{TN}) \geq 0 .$$

$$v_{GS} = V_{GS} + v_{gs}, i_{DS} = I_{DS} + i_{ds}$$

$$I_{DS} + i_{ds} = \frac{K_n}{2}(V_{GS} + v_{gs} - V_{TN})^2$$

$$I_{DS} + i_{ds} = \frac{K_n}{2}\{(V_{GS} - V_{TN})^2 + 2v_{gs}(V_{GS} - V_{TN}) + v_{gs}^2\}$$

DC drain current is

$$I_{DS} = \frac{K_n}{2}(V_{GS} - V_{TN})^2$$

$$i_{ds} = \frac{K_n}{2}\{v_{gs}[2(V_{GS} - V_{TN}) + v_{gs}]\}$$

For i_{ds} to be linearly proportional to v_{gs} , we need $v_{gs} \ll 2(V_{GS} - V_{TN})$.

We can use a factor of 10 to satisfy the inequality, so we get, $v_{gs} = 0.2(V_{GS} - V_{TN})$.


Also,

$$\frac{i_{ds}}{I_{DS}} = \frac{g_m v_{gs}}{I_{DS}} = \frac{I_{DS}}{(V_{GS} - V_{TN})/2} \cdot 0.2(V_{GS} - V_{TN}) \cdot \frac{1}{I_{DS}}.$$

Therefore, a change of $0.2(V_{GS} - V_{TN})$ causes a 40% change in drain and source currents from their quiescent values.

Body-Effect in Four-Terminal MOSFET

please read the body effect part

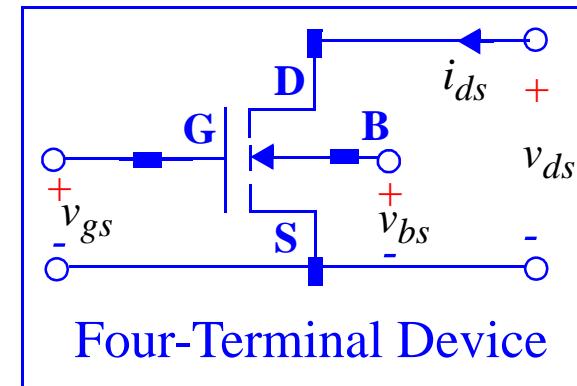


Summary of MOSFET Small-Signal Parameters

Parameter	MOSFET
Transconductance g_m	$\frac{I_{DS}}{(V_{GS} - V_{TN})/2}$ $K_n(V_{GS} - V_{TN})(1 + \lambda V_{DS})$ $\sqrt{2K_n I_{DS}(1 + \lambda V_{DS})}$
Input Resistance	∞
Output Resistance r_o	$\frac{(1/\lambda) + V_{DS}}{I_{DS}}$
Amplification Factor μ_f	$\left\{ \frac{1}{\lambda} + V_{DS} \right\} / \left(\frac{V_{GS} - V_{TN}}{2} \right)$ $\approx \frac{1}{\lambda} \cdot \sqrt{\frac{2K_n}{I_{DS}}} = \frac{2}{\lambda(V_{GS} - V_{TN})}$
Small-Signal Requirement	$v_{gs} \leq 0.2(V_{GS} - V_{TN})$

The small signal model of the PMOS transistor is identical to that of the NMOS transistor.

PSPICE EXAMPLE

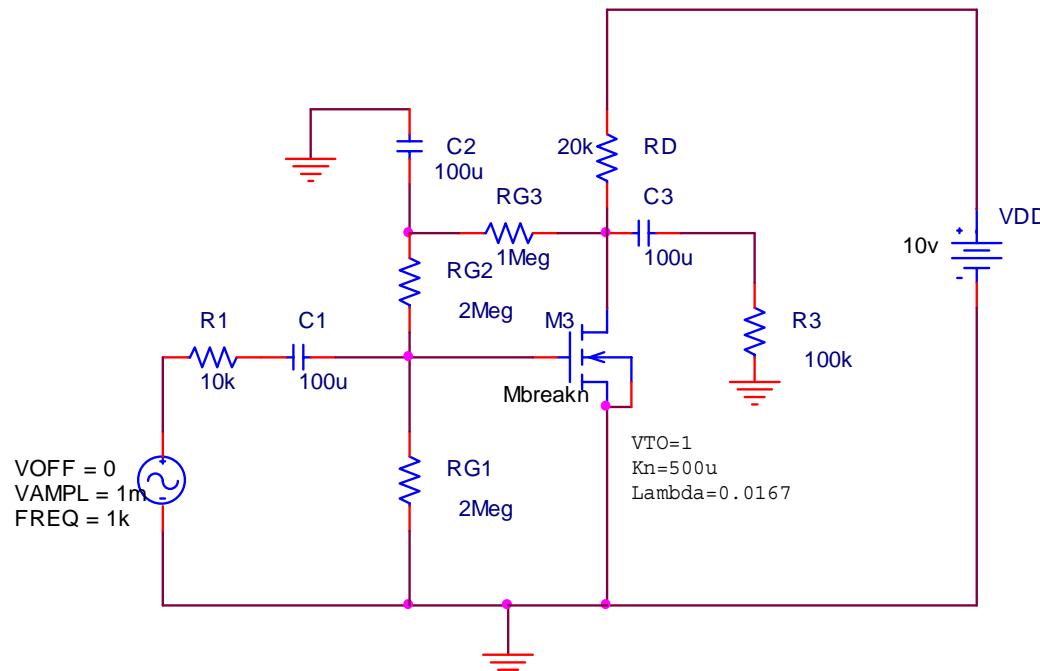

*Libraries:

* Local Libraries :

.LIB ".\example8.lib"

* From [PSPICE NETLIST] section of C:\Program Files\OrcadLite\PSpice\PSpice.ini file:

.lib "nom.lib"

*Analysis directives:

.TRAN 0 20ms 0 10u

.PROBE V(*) I(*) W(*) D(*) NOISE(*)

PSPICE EXAMPLE (Cont'd)

```
.INC ".\example8-SCHEMATIC1.net"
**** INCLUDING example8-SCHEMATIC1.net ****
* source EXAMPLE8

R_RG1      0 N00114 2Meg
R_R3       0 N00510 100k
M_M3       N00072 N00114 0 0 Mbreakn
C_C2       N00186 0 100u
R_RD       N00072 N00350 20k
V_VDD      N00350 0 10v
R_RG3      N00186 N00072 1Meg
C_C1       N006390 N00114 100u
R_R1       N00748 N006390 10k
R_RG2      N00114 N00186 2Meg
C_C3       N00072 N00510 100u
V_Vin     N00748 0
+SIN 0 1m 1k 0 0 0
**** RESUMING example8-SCHEMATIC1-Example7Profile.sim.cir ****
.END
```

PSPICE EXAMPLE (Cont'd)

**** MOSFET MODEL PARAMETERS

Mbreakn

NMOS

LEVEL 1

L 100.000000E-06

W 100.000000E-06

VTO 1

KP 500.000000E-06

GAMMA 0

PHI .6

LAMBDA .0167

**** INITIAL TRANSIENT SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(N00072)	4.9182	(N00114)	1.9673	(N00186)	3.9345	(N00350)	10.0000
(N00510)	0.0000	(N00748)	0.0000	(N006390)	0.0000		

PSPICE EXAMPLE (Cont'd)

VOLTAGE SOURCE CURRENTS

NAME CURRENT

V_VDD -2.541E-04

V_Vin 0.000E+00

TOTAL POWER DISSIPATION 2.54E-03 WATTS

JOB CONCLUDED

TOTAL JOB TIME .39

