

$$5 = I_E \times 1k + 0.7 + I_B \times 10k$$

$$5 = 31 I_B \times 1k + 0.7 + 10k \times I_B$$

$$4.3 = 41 I_B \Rightarrow I_B = 0.104 \text{ mA}$$


$$I_E = 3.25 \text{ mA} \quad , \quad I_C = 3.12 \text{ mA}$$

$$V_B = 10k \times I_B = 1.04 \text{ V}$$

$$V_C = -5 + I_C \times 10 = 25 \leftarrow \text{rejected}$$

\therefore transistor must be saturated
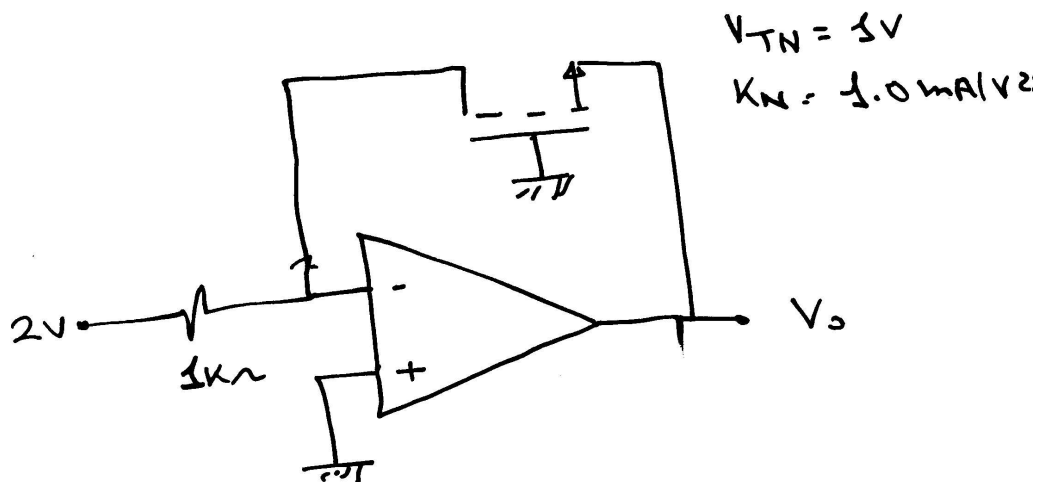
$$\therefore V_{EC} = V_{EC \text{ SAT}} = 0.2 \text{ V}$$



Q. If $V_i = 2V$, what is V_o ?

Answer: transistor must be on and in saturation region (why)


$$I = \frac{2}{5k} = 2 \mu A = I_{D_S}$$

$$\therefore 2 = \frac{K_N}{2} (V_{GS} - V_{TN})^2$$

$$4 = (V_{GS} - 1)^2 \quad (V_{GS} - 1) = \pm 2$$

$$\therefore V_{GS} = 3V$$


$$\therefore V_o = -3V$$

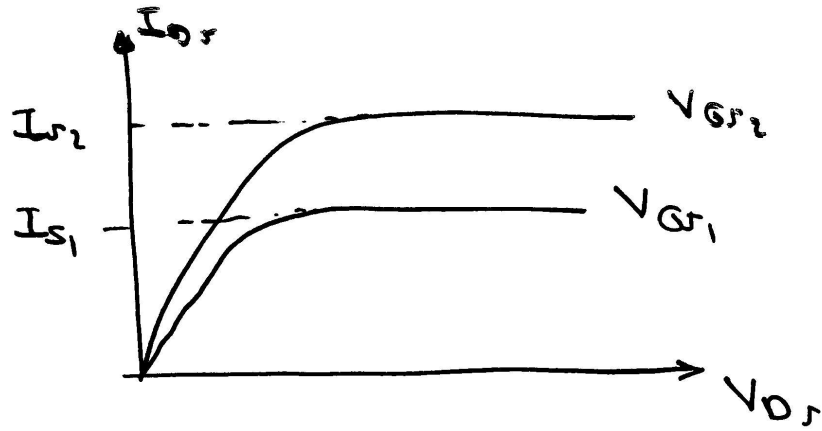


$$I_{S1} = \frac{K_n}{2} (V_{GS1} - V_{TN})^2$$

$$I_{S2} = \frac{K_n}{2} (V_{GS2} - V_{TN})^2$$


Solve for K_n & V_{TN}

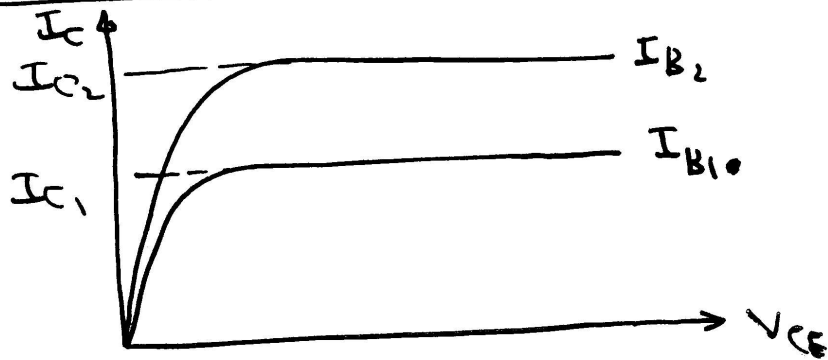

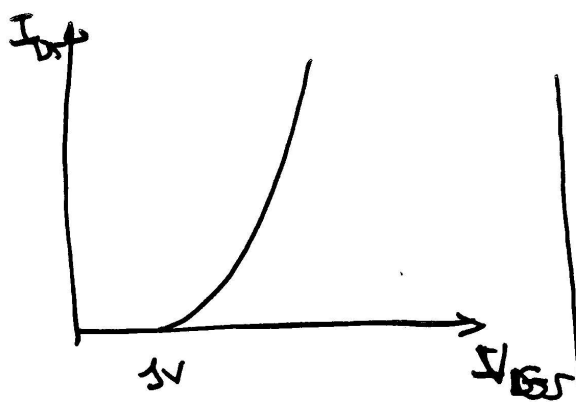
$$\beta = \frac{I_{C1}}{I_{B1}} = \frac{I_{C2}}{I_{B2}}$$




enhancement NMos

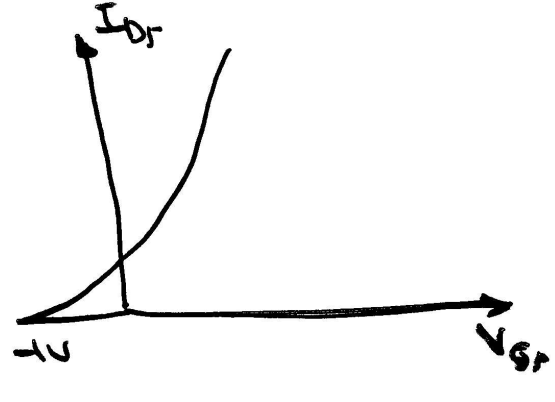


Depletion NMos

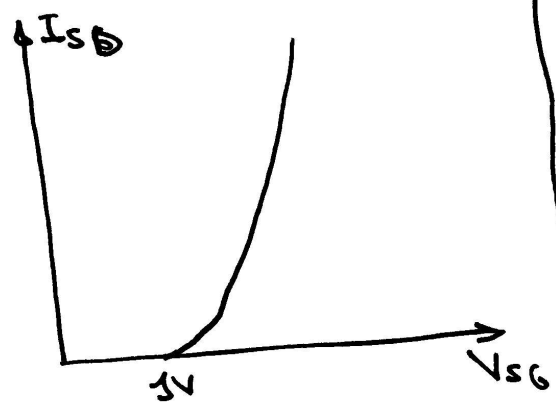

~~Depletion~~ Enhancement PMos

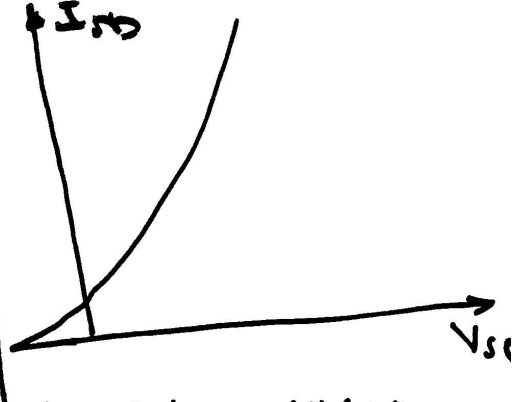

Depletion PMos

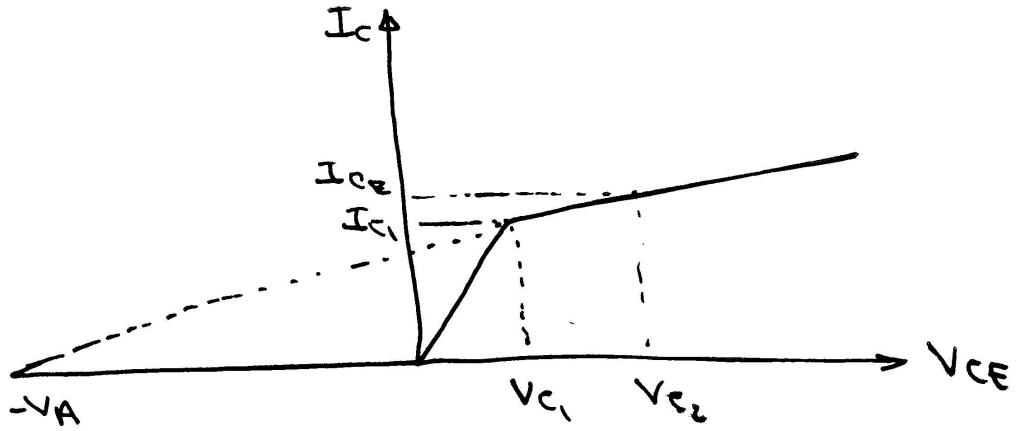

$$\frac{y - y_1}{x - x_1} = \frac{y_2 - y_1}{x_2 - x_1}$$

$$\frac{y - I_{c1}}{V_{ce} - V_{c1}} = \frac{I_{c2} - I_{c1}}{V_{c2} - V_{c1}}$$

~~y = I_{c2}~~ put y = 0 to get V_{ce} = -V_f