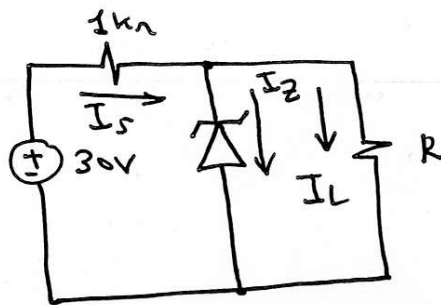


①



$$V_Z = 5V$$

$$R_Z = 0\Omega$$


$$V_{D, on} = 0.7$$

What is the smallest value of R so that the Zener will function as a voltage regulator?

The smallest possible value

of R will make $V_D = -V_Z$

and $I_D = I_Z = 0A$.

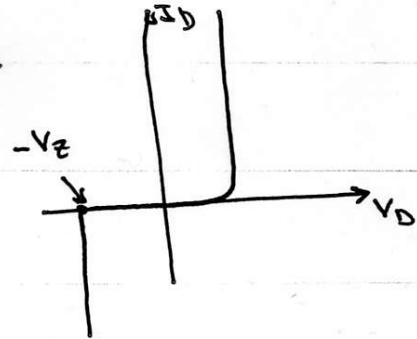


But as $I_s = I_Z + I_L \xrightarrow{\text{at } R_{min}} I_s = I_L$

$$I_s = \frac{30 - 5}{1k} = 25mA = I_L$$

$$\therefore R_{min} = \frac{5V}{25mA} = 0.2k\Omega$$

(2)

If $R_L = 1k\Omega$

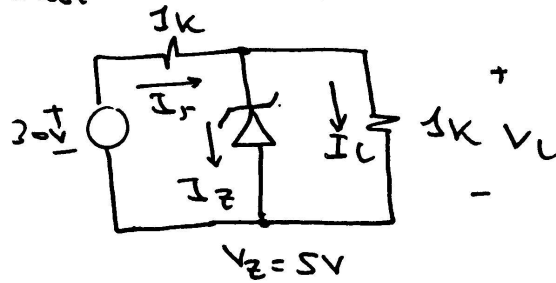

* Assume diode is in reverse region

$$\therefore I_L = I_r = \frac{30}{2k} = 15 \text{ mA} \Rightarrow V_D = -I_L \times R_L$$


$$\therefore V_D = -15V \Rightarrow \text{Contradiction as } V_D < -V_Z$$

* Zener must be in the breakdown region


$$\therefore V_L = 5V \Rightarrow I_L = \frac{5}{1k} = 5 \text{ mA}$$

$$I_r = \frac{30 - 5}{1k} = 25 \text{ mA}$$
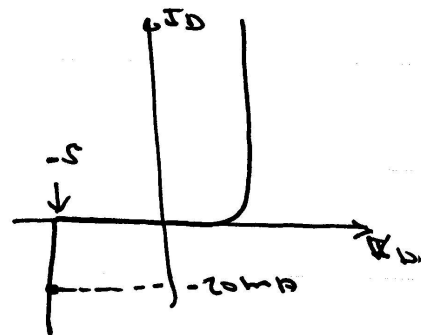
$$\therefore I_Z = I_r - I_L = 20 \text{ mA}$$




B)

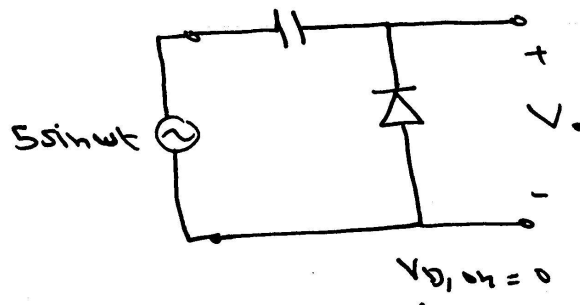

What are the minimum and maximum values of the output voltage V_o ?

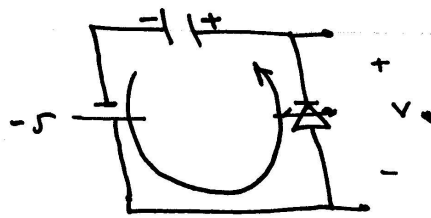
Transient analysis: At the first negative side of the sin wave, diode is forward bias and Capacitor charges to 5V and $V_o = 0V$



Notice that Capacitor CAN NOT discharge.


(4)

Steady state:


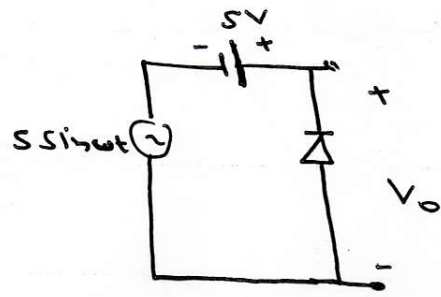


At steady state $V_o = 5 \sin \omega t + 5$, diode is always reverse biased and capacitor can not

discharge

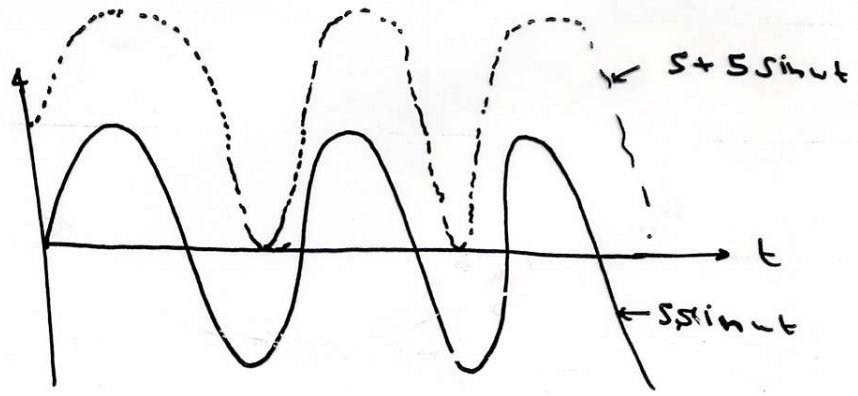

Tr >:

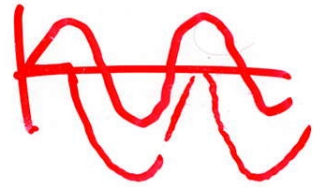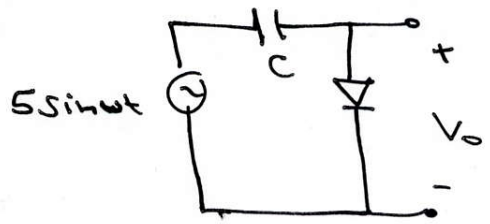


(5)

A pn junction can be approximated by an abrupt junction with $N_A = 10^{18} \text{ cm}^{-3}$, $N_D = 10^{14}$ and $n_i = 10^{10} \text{ cm}^{-3}$. If the width of the depletion region in the n region is 3.0 μm . What is the width of the depletion region in the p region?

$$x_p = \frac{3.0 \times 10^{-6}}{10^4} = 3 \times 10^{-10} \text{ m} = 3 \times 10^{-8} \text{ cm}$$

(using $N_A x_p = N_D x_n$)

(6)

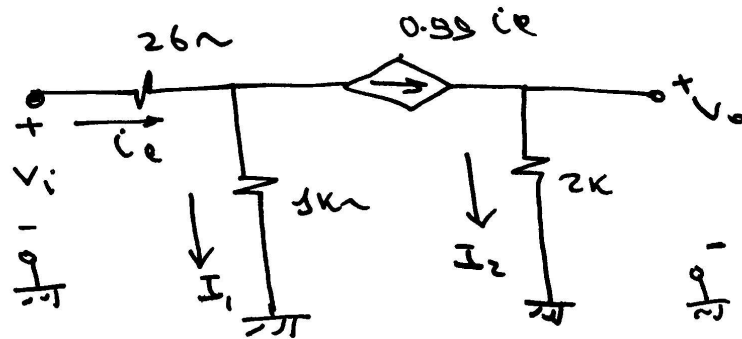

For the shown circuit determine the voltage gain V_o/V_i

$$I_1 = i_e - 0.99 i_e = 0.01 i_e$$

$$V_i = 26 i_e + 1000 \times 0.01 i_e = 36 i_e$$

$$V_o = 0.99 i_e \times 2000$$

$$\therefore \frac{V_o}{V_i} = \frac{0.99 \times 2000}{36} = 55$$