

Student name:

ID Number:

ECE 2EI4 Quiz 1

1) An 8 bit analog to digital converter has a reference voltage of $V_{ref} = 10.24$ V. If the input voltage is 3.34 V, the corresponding output word and the sign of the quantization error are


- a) 01010010, +ve b) 01010100, +ve c) 01010100, -ve d) 01010010, -ve
e) 01010101, +ve

2) The frequency expression of a low-pass voltage amplifier with a mid-band gain of 40 dB and a cut-off frequency of 5 MHz is

- a) $\frac{10^8 \pi s}{(s + 10^7 \pi)}$ b) $\frac{10^8 \pi}{(s + 10^7 \pi)}$ c) $\frac{100}{(s + 10^7 \pi)}$ d) $\frac{10^9 \pi}{(s + 10^7 \pi)}$ e) $\frac{40}{(s + 10^7 \pi)}$

3) The figure to the right shows the transfer function of a voltage amplifier. What are the values of V_a and V_b , respectively, such that the amplifier has a maximum gain of 32 dB and can linearly amplify ac signals with amplitudes up to 0.05 V without distortion?

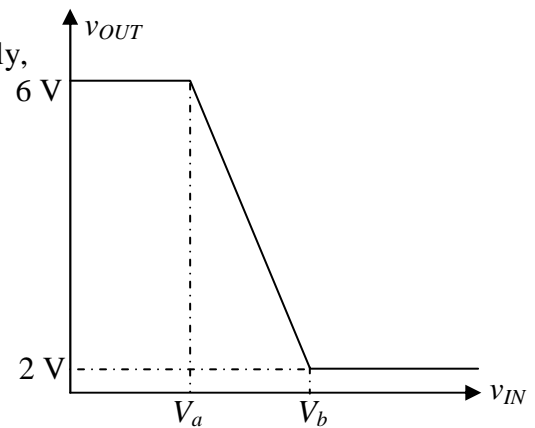- a) 0.2 V, 0.35 V
b) 0.2 V, 0.3 V
c) 0.2 V, 0.25 V
d) 0.25 V, 0.3 V
e) 0.05 V, 0.10 V




4) We have to choose an appropriate amplifier for a sensor application. The input voltage is 1.0 mV in series with a source resistance of 50 K Ω . To obtain $v_{ID} \geq 0.99$ mV, the input resistance of the amplifier should satisfy

- a) $R_{ID} \leq 4.95$ M Ω b) $R_{ID} \leq 5$ M Ω c) $R_{ID} \geq 6$ G Ω
d) $R_{ID} \geq 5$ M Ω e) $R_{ID} \geq 4.95$ M Ω

5) The Thevenin's equivalent voltage and resistance seen between point a and point b are approximately

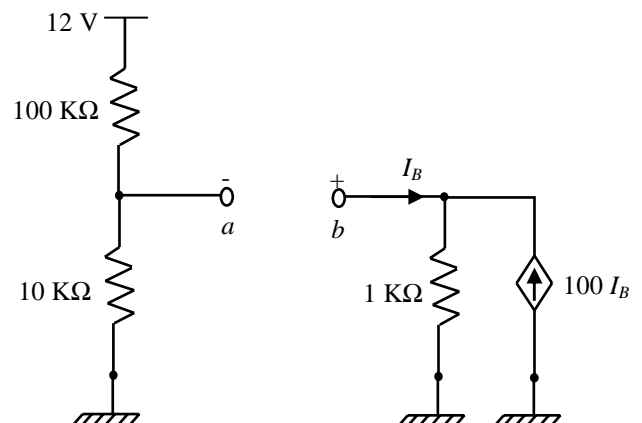- a) 1.09 V, 111 K Ω
b) 1.09 V, 12.1 K Ω
c) 0.12 V, 120 K Ω
d) 0.12 V, 11 K Ω
e) 10.9 V, 99 K Ω



Student name:


ID Number:

6) The g-parameter representation of a two port network is given by:

$$i_1 = g_{11} v_1 + g_{12} i_2$$

$$v_2 = g_{21} v_1 + g_{22} i_2$$

What is g_{21} for the shown circuit?

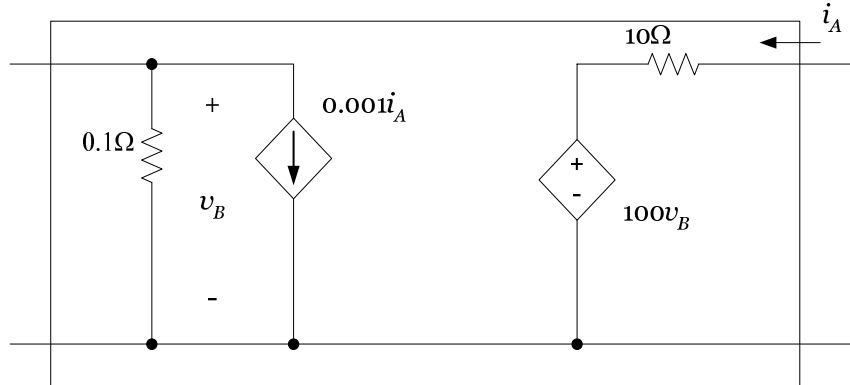


- a) 100 V/V
d) 0.001 A/A

- b) 10 Ohm
e) 0.1 Ohm


- c) 10 S

7) You are asked to design an amplifier with input resistance $\geq 20k$ and a negative gain with amplitude of 100. Which of the designs below meets these criteria?

a)

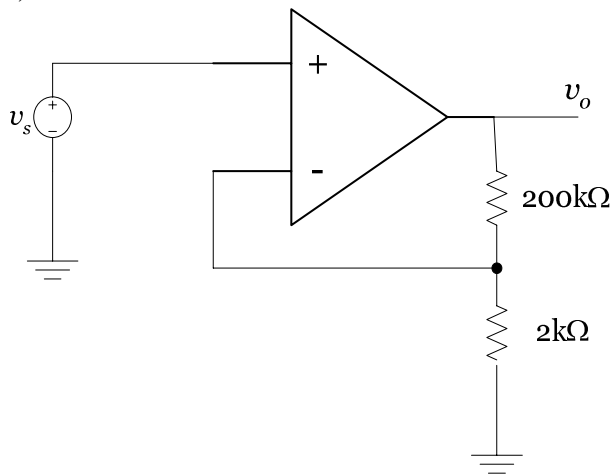


b)

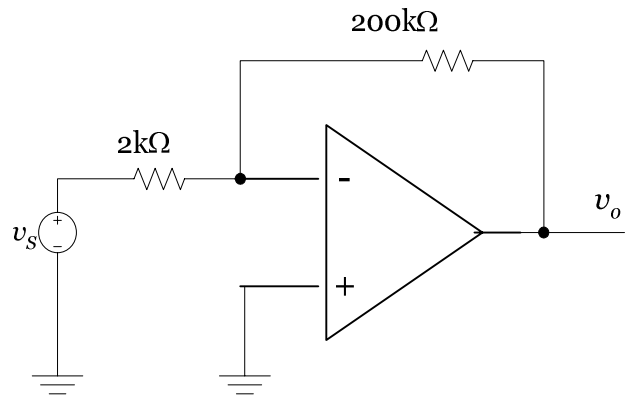


Student name:

ID Number:


c)

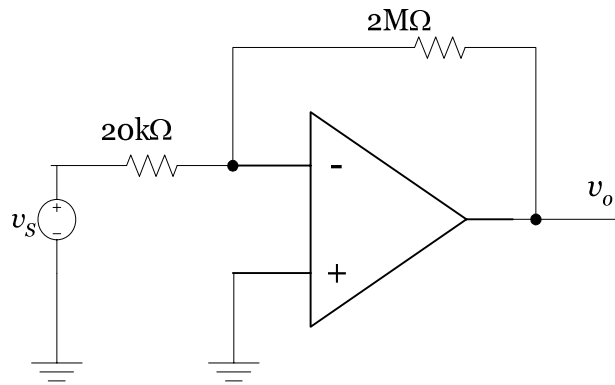

d)

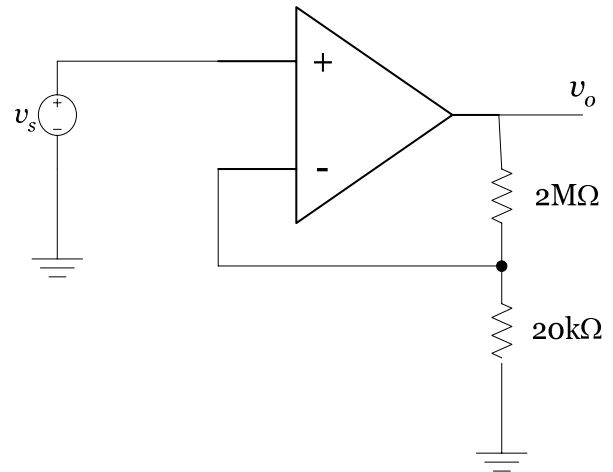

e)

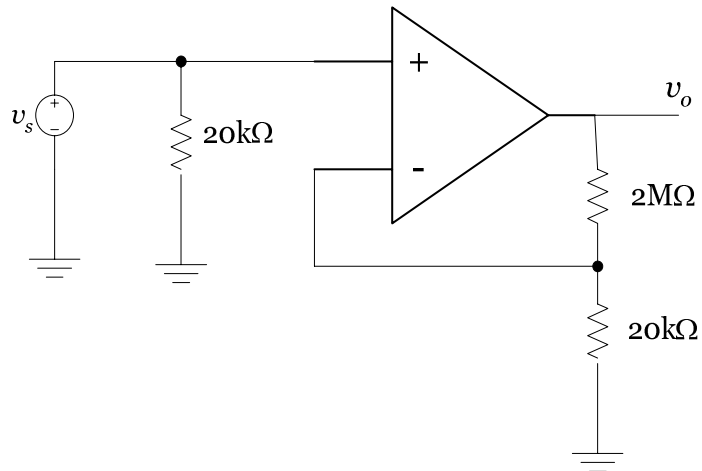

8) Consider the below circuit shown below. The magnitude and phase of the voltage gain are


a) $200, 0^\circ$
d) $201, 90^\circ$

b) $201, 0^\circ$
e) $201, 180^\circ$


c) $200, 180^\circ$

Student name:

ID Number:

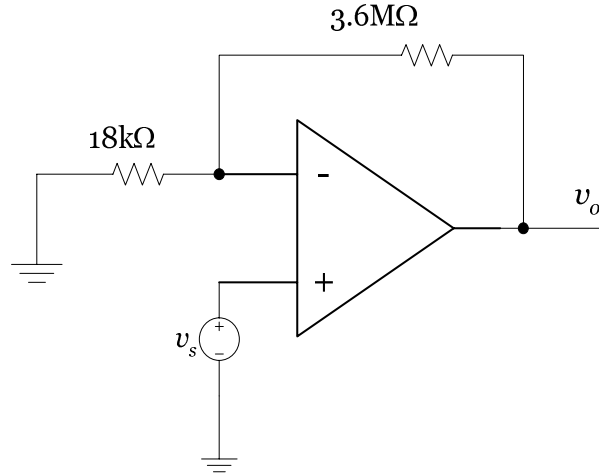

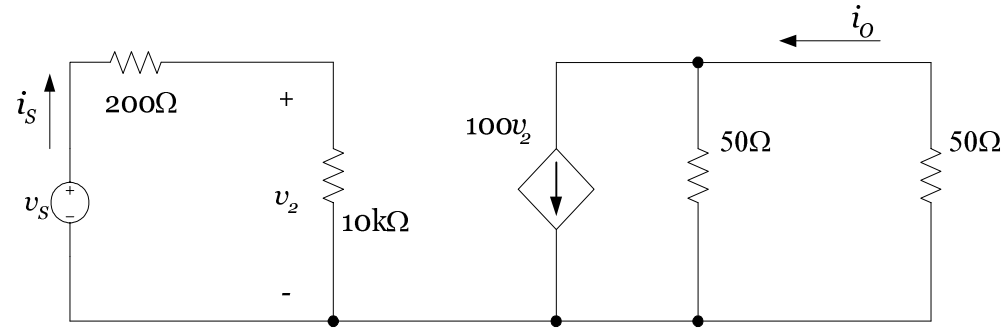
9) In the circuit below, the total forward transconductance (i_o/v_s) is given by:




- a) 101 b) 100 c) 50 d) 98 e) 49

10) Below, you are shown five source circuits. Identify the one case where the use of a unity gain non-inverting amplifier is required in order to deliver a drive current $> 50\mu\text{A}$ to a 100 ohm load.


a)

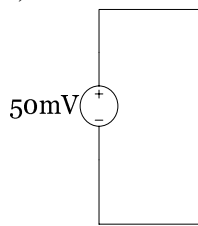

b)

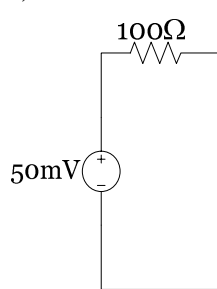


c)

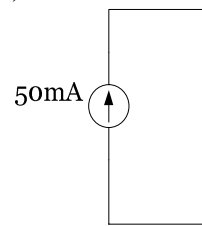

Student name:

ID Number:

d)

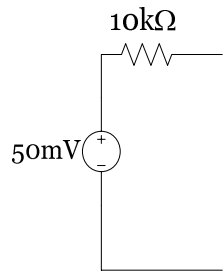

e)

