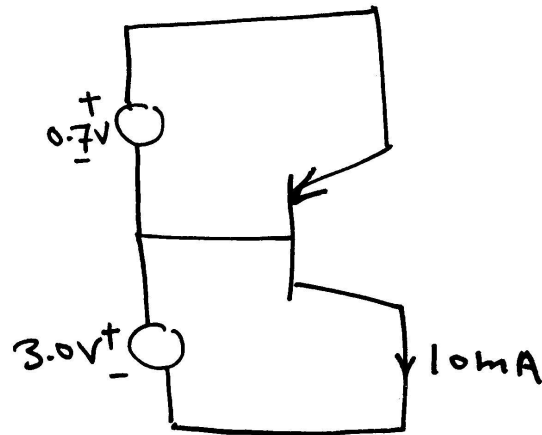


①



Find the value of the transistor Saturation Current


Answer: $V_{EB} = 0.7 > 0$ BE Junction is Forward-biased

* $V_{BC} > 0$ BC Junction is Reverse-biased

* Transistor is in Forward active region $\Rightarrow I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right)$

$$\therefore 10\text{mA} = I_S \exp\left(\frac{0.7}{0.025}\right) \Rightarrow I_S = 6.9 \times 10^{-15} \text{A}$$

(2)

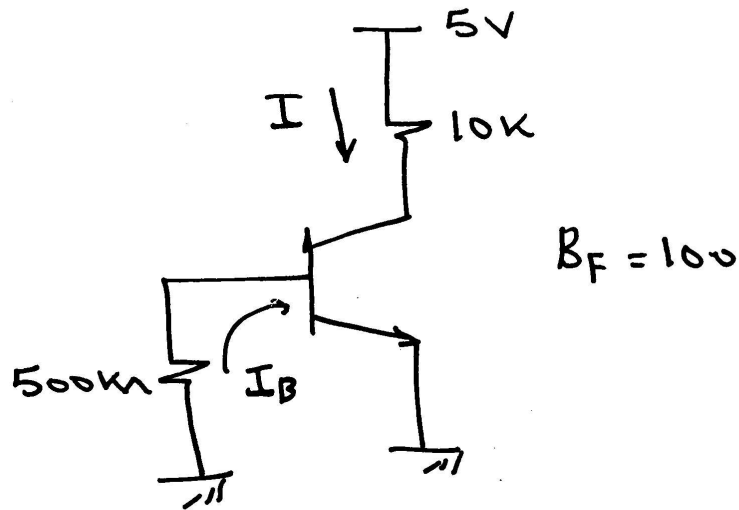

Find the current I for the shown circuit.


* Battery is trying to push current in the shown direction \Rightarrow transistor either in cut-off \Rightarrow Forward active region or Saturation region

* If transistor in Forward active or Saturation $\Rightarrow V_B = -I_B \times 500k < V_E$

$\therefore V_{BE} < 0 \Rightarrow$ Contradiction

\therefore transistor is off and $I = 0A$

(3)

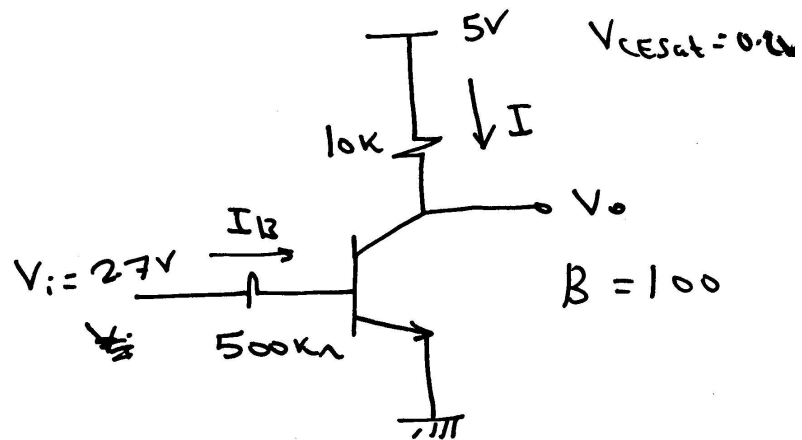

Find the current I for $V_i = 0, 2.7V$
and $5V$

* For $V_i = 0V$, transistor must be off
 $I = 0A$

* For $V_i = 2.7V$, we assume Forward active
region

$$I_B = \frac{2.7V - 0.7V}{500K} = 4\mu A$$

$$I_C = \beta I_B = 0.4\mu A$$

$$V_C = V_o = 5 - 0.4 \times 10^{-3} \times 10^4 = 1V$$

$\therefore V_C > V_B \Rightarrow BC$ Junction is reverse biased

(4)

Our assumption is valid

* For $V_i = 5V$

Assuming forward active region

$$I_B = \frac{5 - 0.7}{500k} = 8.6 \mu A$$

$$I_C = \beta I_B = 100 \times 8.6 \mu A = 0.86 mA$$

$$\therefore V_C = 5 - 0.86 \times 10 = -3.6 \Rightarrow \text{reject}$$


It follows that transistor is saturated

$$\text{and } V_{CE} = V_{CEsat} = 0.2V$$

$$I_C = \frac{5 - 0.2}{10k} = 0.48 mA$$

Notice that $I_C < \beta I_B$ for saturation region

(5)

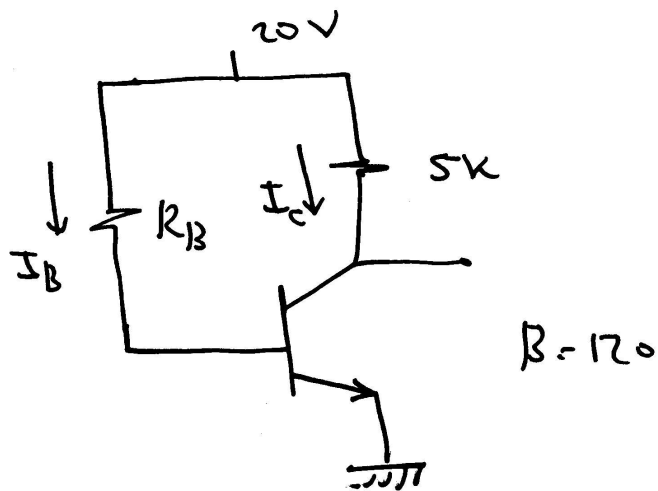

Find R_B such that $V_{CEQ} = 10V$
Transistor is in forward active region

$$I_C = \frac{20 - 10}{5k} = 2mA$$

$$I_B = \frac{I_C}{\beta} = \frac{2mA}{120} = 16.66\mu A$$

$$\text{But } I_B = \frac{20 - 0.7}{R_B} \Rightarrow R_B = \frac{19.3 \times 10^3}{16.6}$$

$$\therefore R_B = 1.16M\Omega$$