

①

An 8 bit A/D Converter has a reference voltage of  $V_{ref} = 10.24$

Find the output word and the corresponding quantization error for  $V_{in} = 3.34V$

Answer:  $\left( \right)$

$$3.34 = (2^{-1}b_1 + 2^{-2}b_2 + \dots + 2^{-8}b_8) 10.24$$

$$\frac{3.34}{10.24} = 2^{-1}b_1 + 2^{-2}b_2 + \dots + 2^{-8}b_8$$

$$\frac{3.34 \times 2^8}{10.24} = b_1 \times 2^7 + 2^6 b_2 + 2^5 b_3 + \dots + b_8$$

$$83.5 = 128 b_1 + 64 b_2 + 32 b_3 + \dots + b_8$$

$$b_1 = 0 \quad b_2 = 1$$

$$19.5 = 32 b_3 + 16 b_4 + 8 b_5 + 4 b_6 + 2 b_7 + b_8$$


$$b_3 = 0, \quad b_4 = 1$$

$$3.5 = 8 b_5 + 4 b_6 + 2 b_7 + b_8$$



$$b_5 = 0, \quad b_6 = 1, \quad b_7 = 0 \quad \& \quad b_8 = 0$$

$$01010100, \quad -ve$$

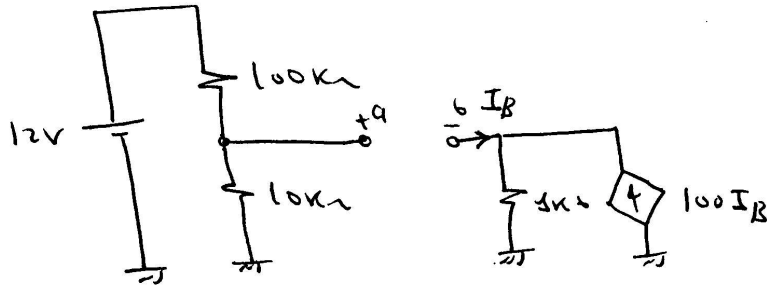②  
Get the Thevenin equivalent between terminals a & b



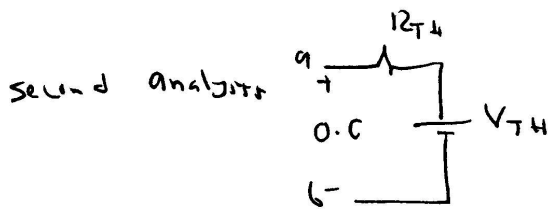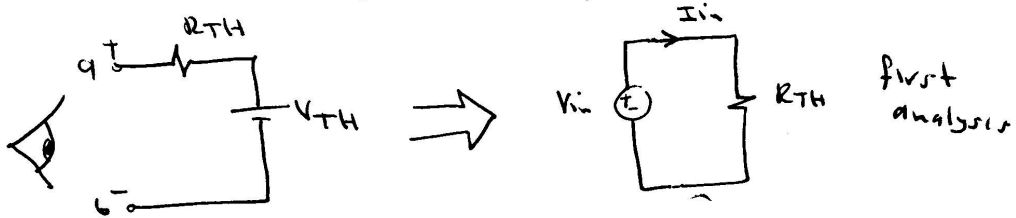
Answer: Two analyses are required to get  $V_{TH}$  &  $R_{TH}$



\* first we get  $V_{TH}$ . As  $I_B = 0 \Rightarrow 100I_B = 0$

$$V_{ab} = V_{TH} = V_a - V_b = 12 \times \frac{10}{110} - 0 = 1.09V$$

\* second we get  $R_{TH}$

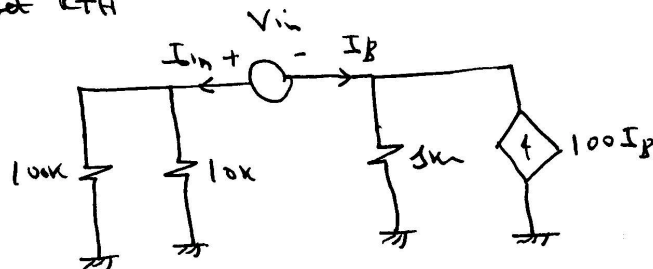

3


$$V_{in} = I_{in} \times (100k // 10k) - 10I_B \times 3k$$

$$= I_{in} \times (100k // 10k) + 10I_{in} \times 3k$$

$$V_{in} = 9.09k \times I_{in} + 30k \times I_{in} = 39.09k \times I_{in}$$


$$\therefore R_{TH} = \frac{V_{in}}{I_{in}} = 39.09k$$

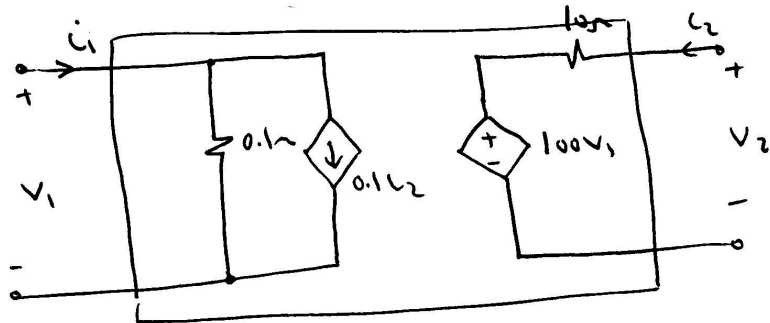Find the h parameters for the shown circuit



$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

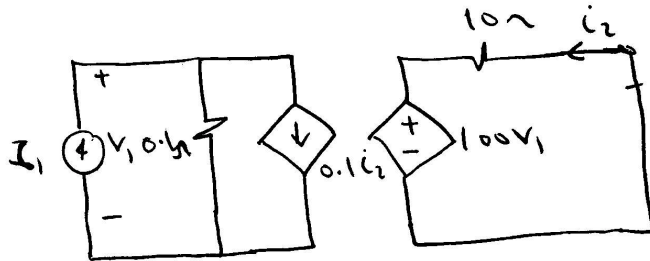\* We first obtain  $h_{11}$  &  $h_{21}$  by setting  $V_2 = 0$



$$i_2 = -10V_1$$


$$V_1 = (I_1 - 0.1i_2) \times 0.1 = (I_1 + 10V_1) \times 0.1$$

$$0.9V_1 = 0.1I_1 \Rightarrow \frac{V_1}{I_1} = h_{11} = \frac{1}{9} = 0.111k$$

$$h_{21} = \frac{i_2}{I_1} = \frac{-10V_1}{I_1} = -10 \times \frac{1}{9} = -1.111$$

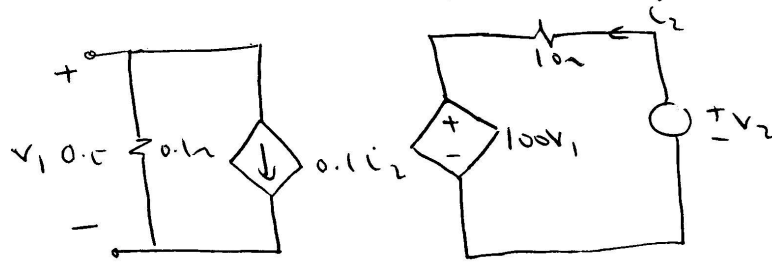(4)

To get  $h_{12}$  &  $h_{22}$  we set  $i_1 = 0$  (o.c. at input)



$$i_2 = \frac{v_2 - 100v_1}{10} \quad \text{but } v_1 = -0.01 i_2$$

$$\therefore i_2 = \frac{v_2 + i_2}{10} \Rightarrow 0.9 i_2 = 0.1 v_2$$

$$h_{22} = \frac{i_2}{v_2} = \frac{1}{9} = 0.111$$

$$h_{12} = \frac{v_1}{v_2} = \frac{v_1}{i_2} \times \frac{i_2}{v_2} = -0.01 \times \frac{1}{9} = -\frac{1}{900} = -1.111 \times 10^{-3}$$


- TF Directive can be used to get  $G, h, Y,$  and  $Z$
- TF  $X_{in}, X_{out}$  ( $X_{in}, X_{out}$  may be current or voltages)

output from .TF

$$\frac{\Delta X_{out}}{\Delta X_{in}}, R_{in}(X_{in}), R_{in}(X_{out})$$

\* By properly selecting  $X_{in}$  &  $X_{out}$  we can get all parameters

Example

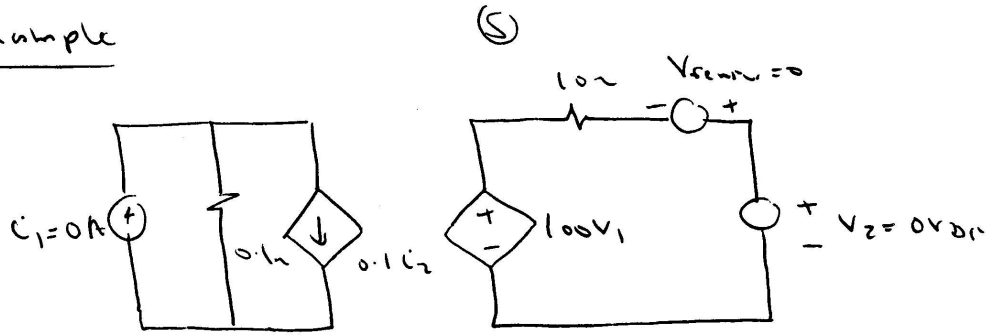

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

\* If  $V_2 = 0$   $V_1 = h_{11} i_1$  &  $i_2 = h_{21} i_1$

$\therefore h_{11} = \frac{V_1}{i_1} = R_{in}(i_1)$  &  $h_{21} = \frac{\Delta i_2}{\Delta i_1}$

So we select  $X_{in} = i_1$  &  $X_{out} = i_2$  ( $V_{sensor}$ )

\* If  $i_1 = 0$   $V_1 = h_{12} V_2$  ,  $i_2 = h_{22} V_2$

$h_{22} = \frac{i_2}{V_2} = \frac{1}{R_{in}(i_2)}$  ,  $h_{12} = \frac{V_1}{V_2} = \frac{\Delta V_1}{\Delta V_2}$

So we select  $X_{in} = V_2$  &  $X_{out} = V_1$

Simulation Settings - TutorialExample4Profile

General Analysis | Include Files | Libraries | Stimulus | Options | Data Collection | Probe Window

Analysis type:

Bias Point

Options:

- General Settings
- Temperature (Sweep)
- Save Bias Point
- Load Bias Point

Output File Options


- Include detailed bias point information for nonlinear controlled sources and semiconductors (.OP)
- Perform Sensitivity analysis (.SENS)  
Output variable(s):
- Calculate small-signal DC gain (.TF)  
From Input source name: V2  
To Output variable: V[1]

OK


Cancel

Apply

Help

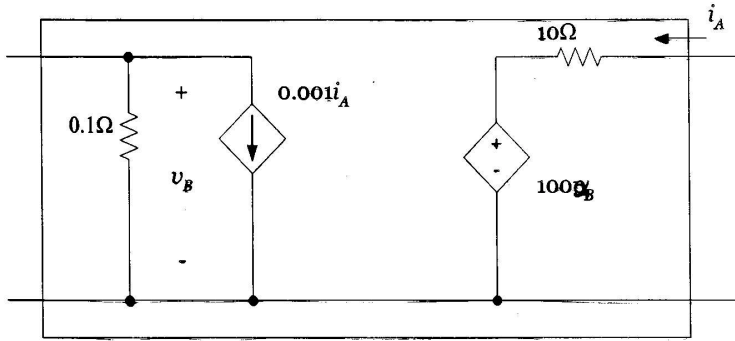

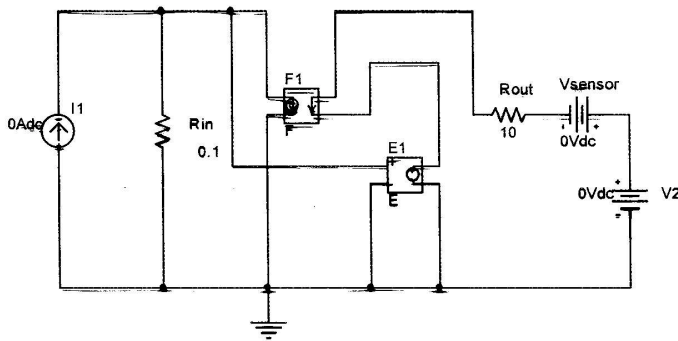calculate the h parameters using the .TF directive in PSpice



The .TF directive is applied twice: first between I1 and I(Vsensor) to get h11 and h21

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

$$I(V\_Vsensor)/I\_I1 = -1.111E+00$$

$$\text{INPUT RESISTANCE AT } I\_I1 = 1.111E-01$$

$$\text{OUTPUT RESISTANCE AT } I(V\_Vsensor) = 9.000E+00$$

The .TF directive is then applied between V2 and V(I1) (notice reverse polarity)

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

$$V(I\_I1)/V\_V2 = 1.111E-03$$

$$\text{INPUT RESISTANCE AT } V\_V2 = 9.000E+00$$

$$\text{OUTPUT RESISTANCE AT } V(I\_I1) = 1.111E-01$$