

Dr. Mohamed Bakr, EE3FK4, 2008

Note Title

3/17/2008

Lecture 15


from Section 11.4 of textbook

Solve 11.17 - 11.26

Transmission Line Circuits

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

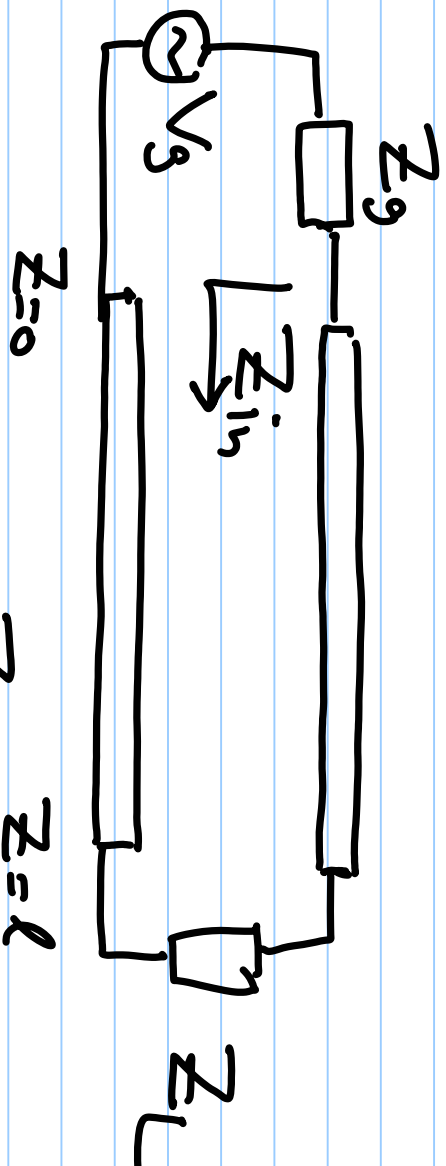
$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}$$



at $z=0$ (Generator Side)

use have
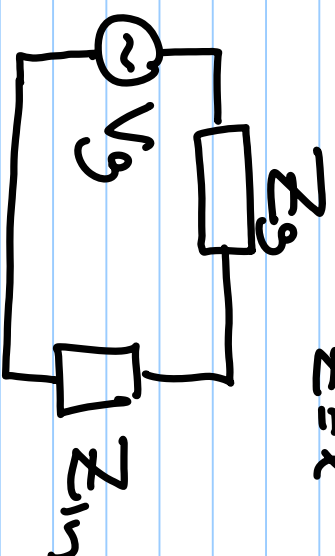
$$V(0) = V_0^+ + V_0^-, \quad I(0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$



Input Impedance

$$Z_{in} = \frac{V(0)}{I(0)} = Z_0 \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right)$$

* Now the circuit looks like a voltage divider

$$V(0) = V_g * \frac{Z_{in}}{Z_{in} + Z_g} \quad \text{and} \quad I(0) = \frac{V_g}{Z_g + Z_{in}}$$

* We can solve for V_0^+ & V_0^- to obtain

$$V_0^+ = \frac{1}{2} (V(0) + Z_0 I(0)), \quad V_0^- = \frac{1}{2} (V(0) - Z_0 I(0))$$

Input Impedance (Cont'd)

* at the Load Side, we have

$$\vec{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}, \quad \vec{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z}$$

$$\text{but } \frac{\vec{V}(z)}{\vec{I}(z)} = Z_L, \quad V_L = \vec{V}(z), \quad I_L = \vec{I}(z)$$

* We can thus express V_0^+ & V_0^- by

$$V_0^+ = \frac{1}{2} (V_L + Z_0 I_L) e^{\gamma z}, \quad V_0^- = \frac{1}{2} (V_L - Z_0 I_L) e^{-\gamma z}$$

Input Impedance (Cont'd)

* at any distance $d < \ell$, we have

$$Z_{in}(d) = \frac{V(d)}{I(d)} = \frac{V_0^+ e^{-\gamma d} + V_0^- e^{\gamma d}}{\frac{V_0^+}{Z_0} e^{-\gamma d} - \frac{V_0^-}{Z_0} e^{\gamma d}}$$

Substituting for V_0^+ & V_0^- and using

$$\cosh \gamma d = \frac{e^{\gamma d} + e^{-\gamma d}}{2} \quad \text{and} \quad \sinh \gamma d = \frac{e^{\gamma d} - e^{-\gamma d}}{2}, \quad \text{we get}$$

Input Impedance formula

$$Z_{in}(d) = Z_0 \left[\frac{Z_L + jZ_0 \tanh \gamma d}{Z_0 + jZ_L \tanh \gamma d} \right]$$

For the lossless case $\gamma = j\beta$


$$Z_{in}(d) = Z_0 \left[\frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} \right]$$




Load Example

* Short Circuit Load $Z_L = 0$
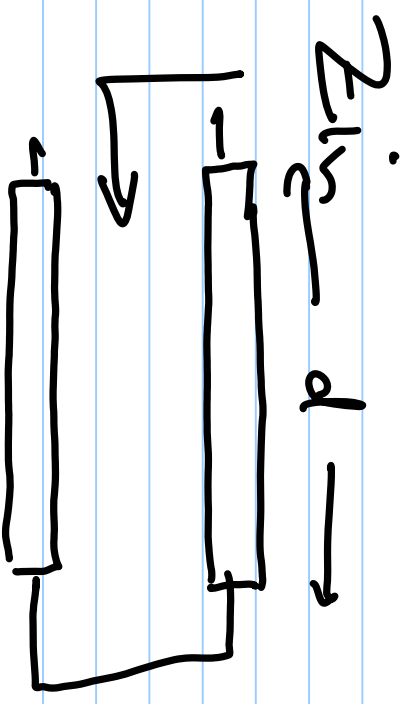
$$\Rightarrow Z_{in}(d) = jZ_0 \tan \beta d$$




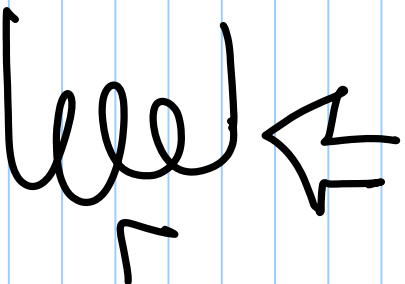This is equivalent to an inductor L , whose value is determined by Z_0 , β , and d



Load Examples (Cont'd)

* Open Circuit Load ($Z_L = \infty$)

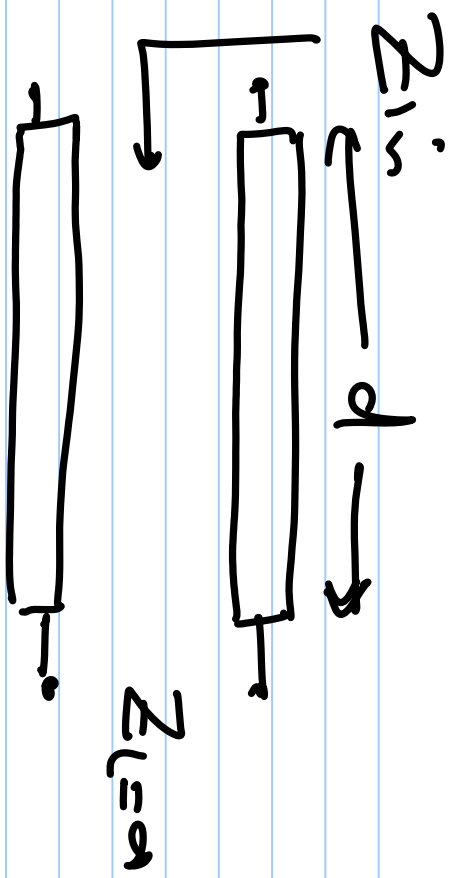


* Using the Impedance formula, we have

$$Z_{in} = -jZ_0 \cot \beta d$$

a Capacitor of value C

where $C = C(Z_0, \beta, d)$

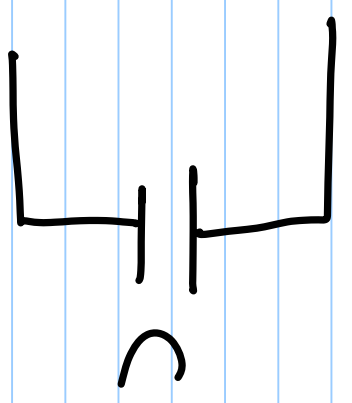

Load Example (Cont'd)


* If $d = \lambda/4$, $\gamma = \frac{2\pi}{\lambda} = \text{wave length}$

$$\Rightarrow R_d = \gamma_c * B = \gamma_c * \frac{2\pi}{\lambda} = \frac{\pi}{2}$$

$$\tan R_d = \infty$$

$$Z_{in}(d) = \frac{Z_0^2}{Z_L}$$

\Rightarrow impedance transformer

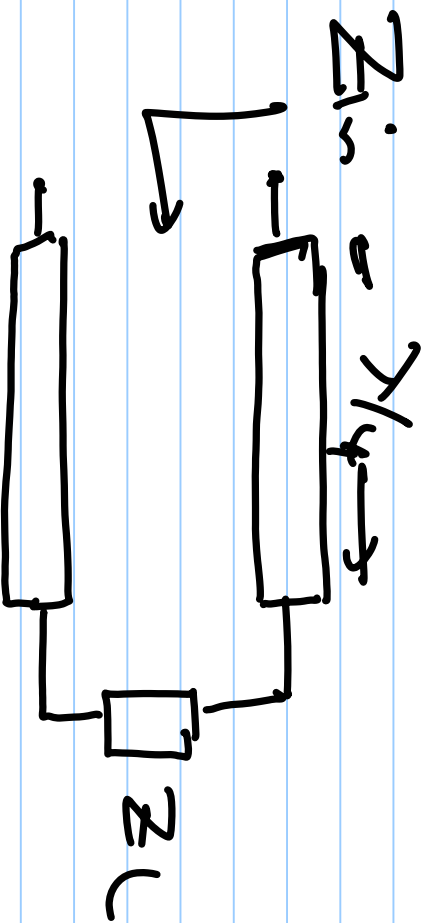

Reflection Coefficient

* It is defined as the ratio of reflected to incident voltage waves

$$\Gamma(r) = \frac{V_0^- e^{j\beta r}}{V_0^+ e^{-j\beta r}}$$

$$\left. \begin{aligned} V_0^+ &= \frac{1}{2} (V_L + Z_0 I_L) e^{j\beta r} \\ V_0^- &= \frac{1}{2} (V_L - Z_0 I_L) e^{-j\beta r} \end{aligned} \right\}$$

Substitutions, we get $\Gamma(r) = \frac{Z_L - Z_0}{Z_L + Z_0}$

Reflection Coefficient (cont'd)

* At any distance d , we have

$$\Gamma(d) = \frac{V_0^- e^{j\omega d}}{V_0^+ e^{-j\omega d}} = \frac{V_0^-}{V_0^+} e^{2j\omega d} = \frac{Z_L - Z_0}{Z_L + Z_0} e^{-2j\omega d} e^{2j\omega d}$$

$$\Gamma(d) = \Gamma e^{-2j\omega d}$$

For a lossless line $|\Gamma(d)| = |\Gamma|$

