

# Logic Design


Flip Flops, Registers and Counters



# Introduction


- Combinational circuits: value of each output depends only on the values of inputs
- Sequential Circuits: values of outputs depend on inputs and past behavior of the circuit
  - Circuit contains storage (memory) elements

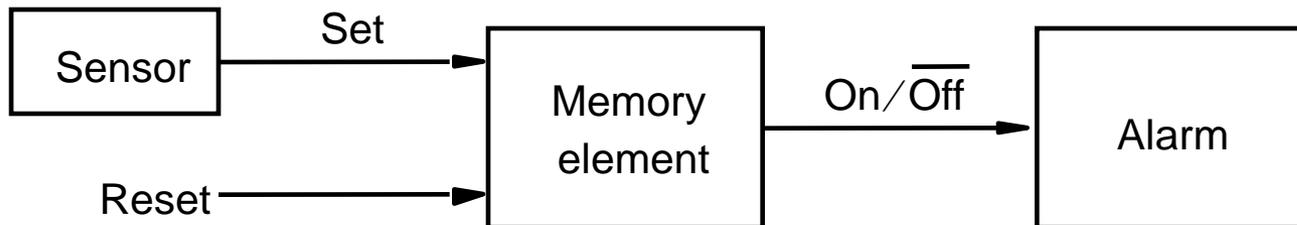- Example: an alarm system in which the alarm stays on when triggered even if the sensor output goes to zero



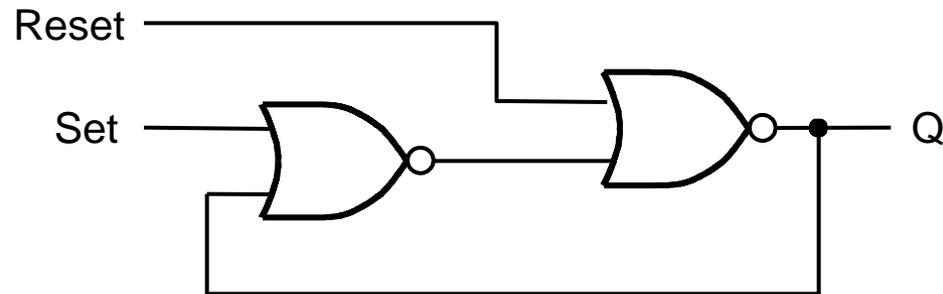
# Basic Latch

- Simplest memory element: basic latch
- Can be built with NAND or NOR gates




# Basic Latch

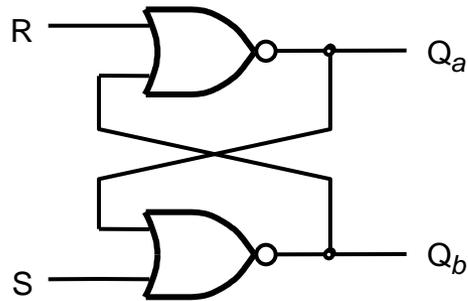

(a) Circuit

S	R	$Q_a$	$Q_b$
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

(b) Truth table

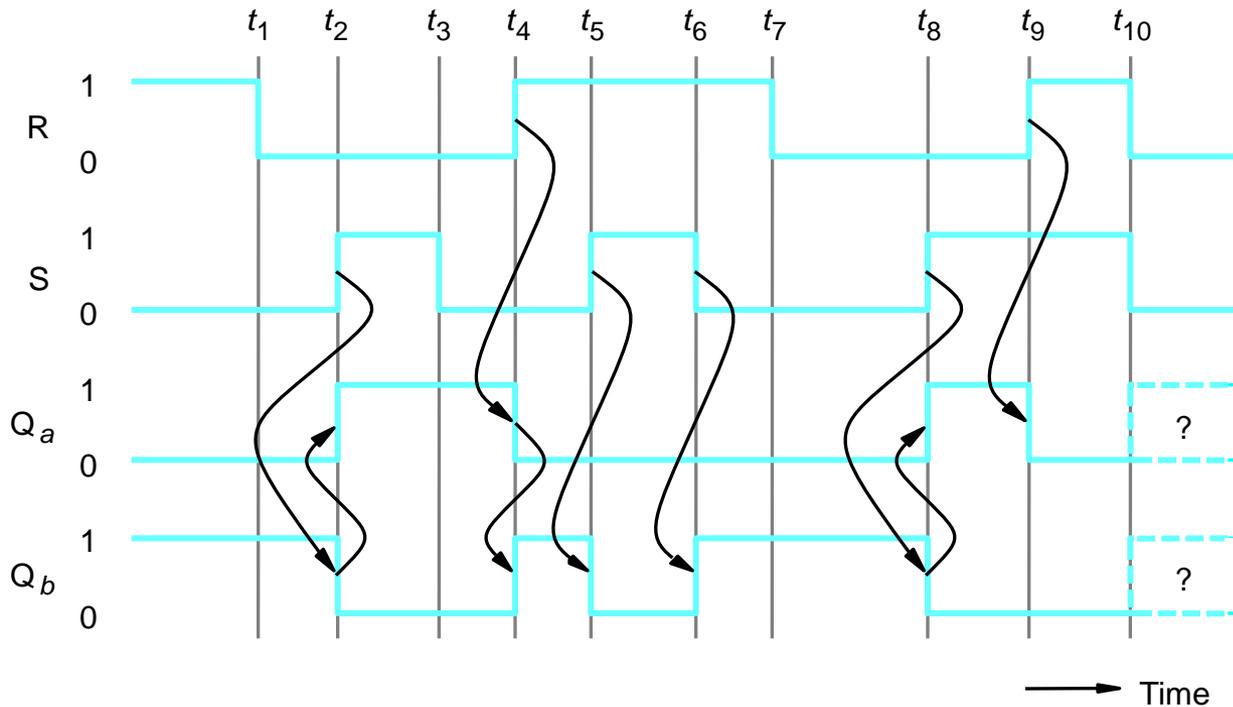


(c) Timing diagram

# Basic Latch

- In basic latch, the state changes when the inputs change
- In many circuits we cannot control when the inputs change but would like the change in state happens at particular times
- We add a clock (clk) signal to the basic latch


# Gated SR Latch

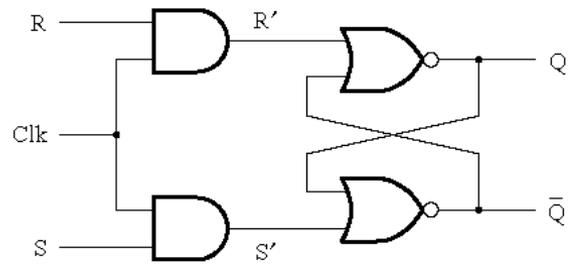


(a) Circuit

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

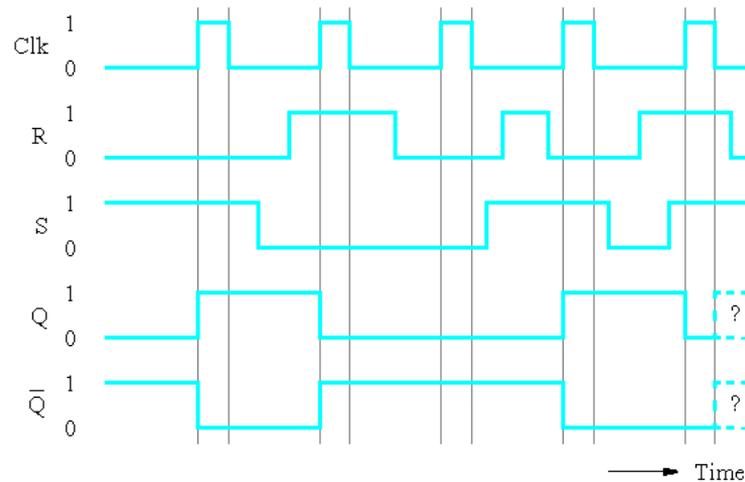


(c) Timing diagram

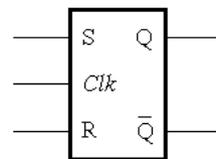

(d) Graphical symbol
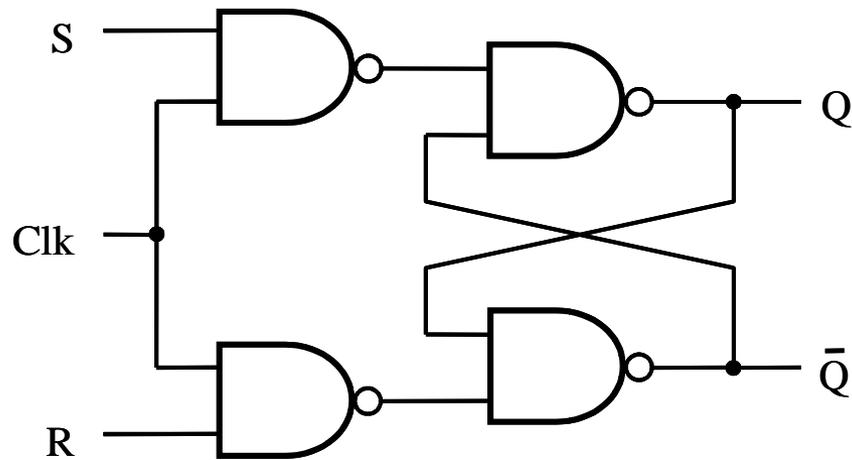
# Gated Latch with NAND


- Behavior of the circuit is the same as the one with NOR
- Clock is gated by NAND gates rather than AND gates
- S and R inputs are reversed



# D latch

- D latch is based on gated SR latch
- Instead of two inputs, has one input


# D Latch

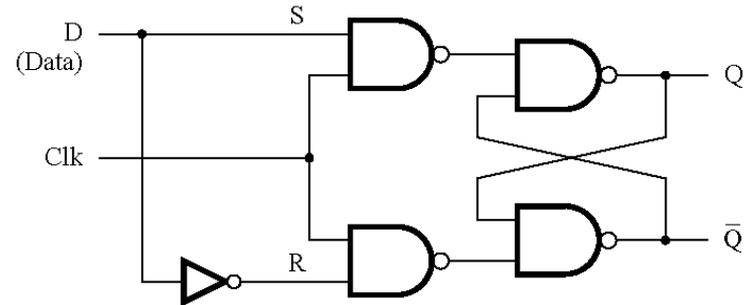


(a) Circuit

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

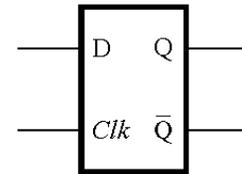

(c) Graphical symbol

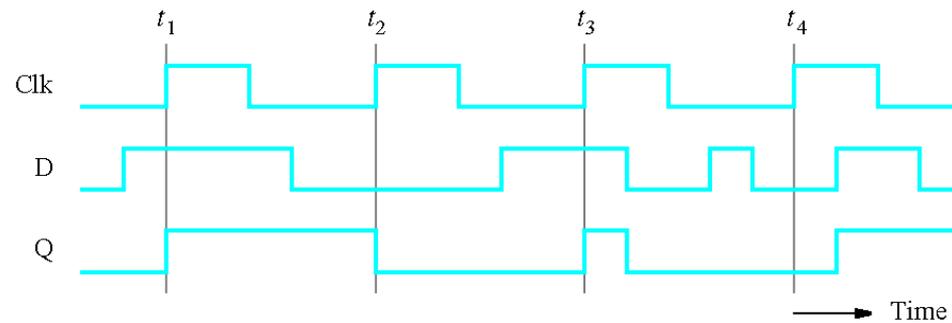


(d) Timing diagram

# D Latch

- Since the output of gated D latch is controlled by the level of clock, it is called level sensitive
  - In the window of  $clk=1$ , the output Q tracks the changes of input D. This is undesirable.
- It is possible to design storage elements for which the output changes only when clock changes from one value to the other.
- Those circuits are called edge triggered
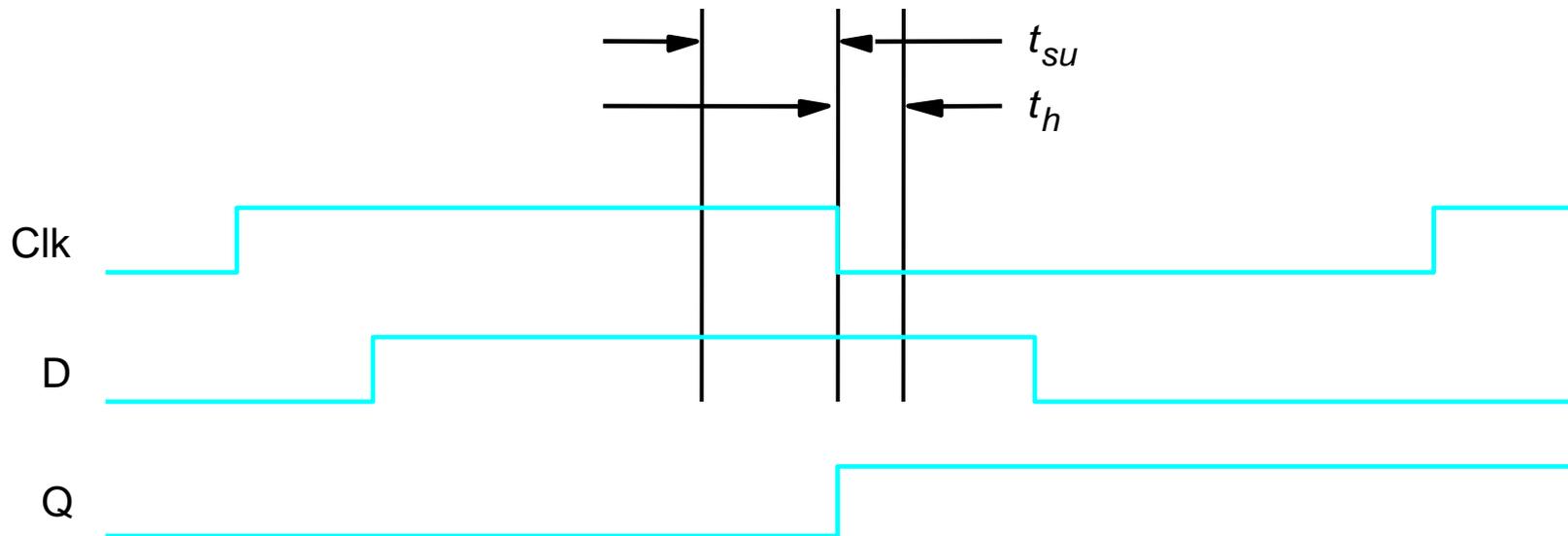
# Propagation delay


- D latch: stores the value of D input at the time clock goes from 1 to 0.
- It operates properly if input is stable (not changing) at the time clk goes from 1 to 0.




# Master-slave D flip-flop

- Master-slave D flip-flop: two gated D latches
- First one, called master, changes its state when  $\text{clk}=1$
- Second one, called slave, changes its state when  $\text{clk}=0$
- From external point of view, master-slave flip-flop changes its state at the negative edge of clock


# Master-slave D flip-flop

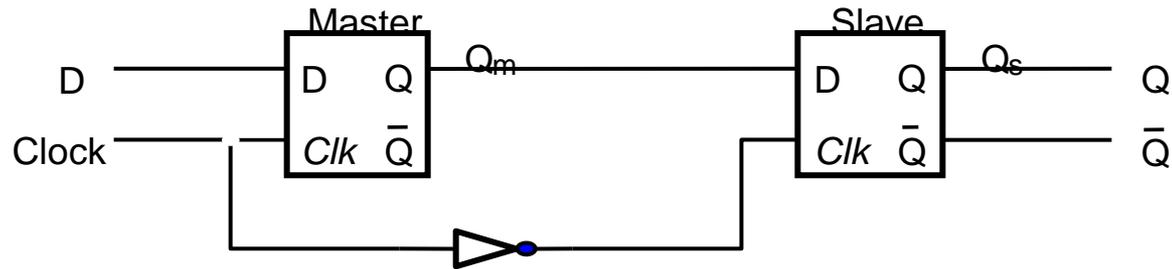

(a) Circuit

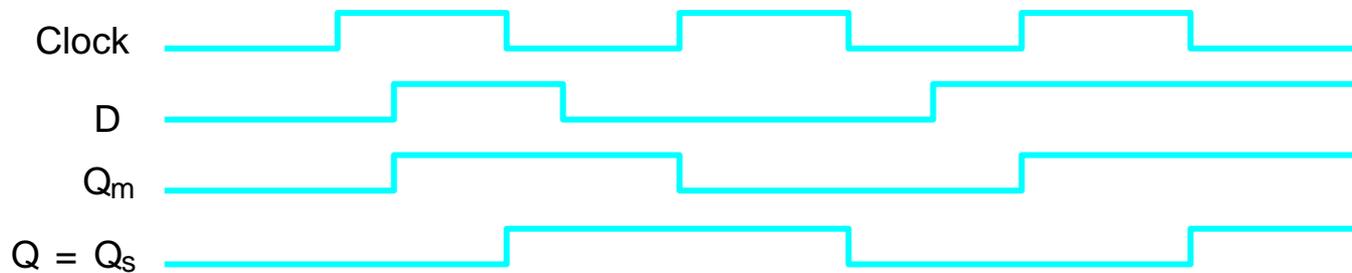


(b) Timing diagram

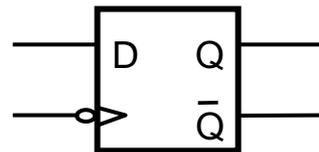


(c) Graphical symbol

# Edge-triggered D flip-flop

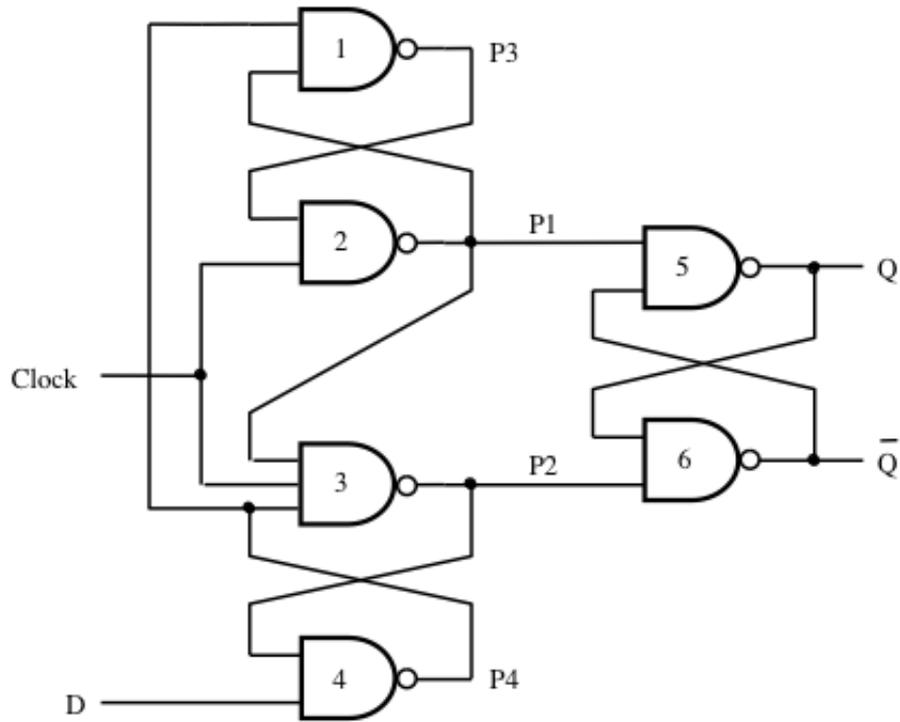

(a) Circuit

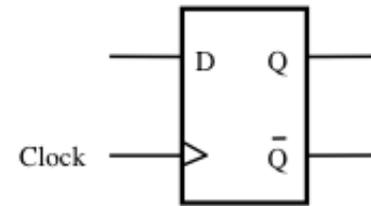


(b) Graphical symbol


Figure 7.11. A positive-edge-triggered D flip-flop.
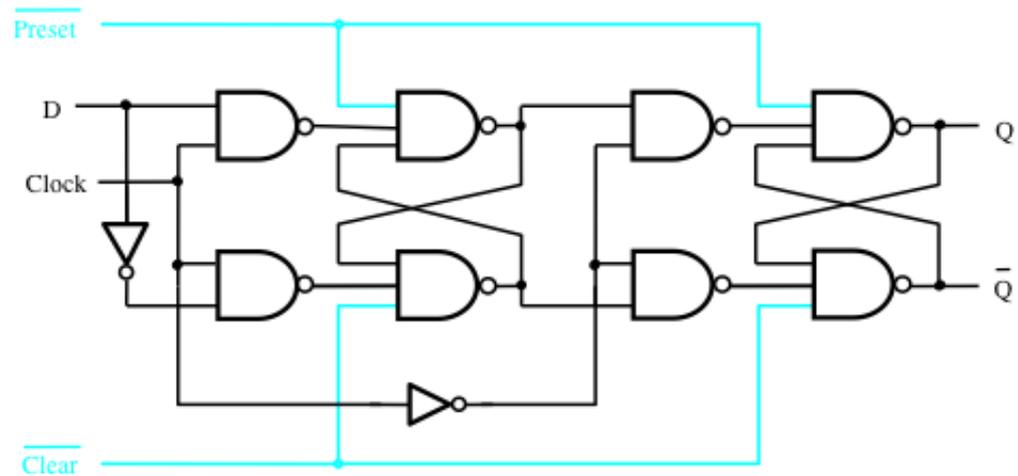
# D flip-flop with clear and preset

- An example of application of flip-flops: counters
- We should be able to clear the counter to zero
- We should be able to force the counter to a known initial count
- Clear: asynchronous, synchronous
- Asynchronous clear: flip-flops are cleared without regard to clock signal
- Synchronous clear: flip-flops are clear with the clock signal




(a) Circuit

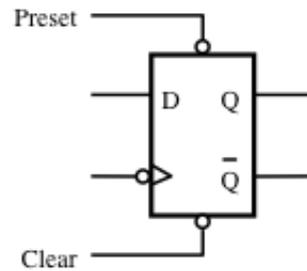


(b) Graphical symbol

Figure 7.13. Master-slave D flip-flop with *Clear* and *Preset*.
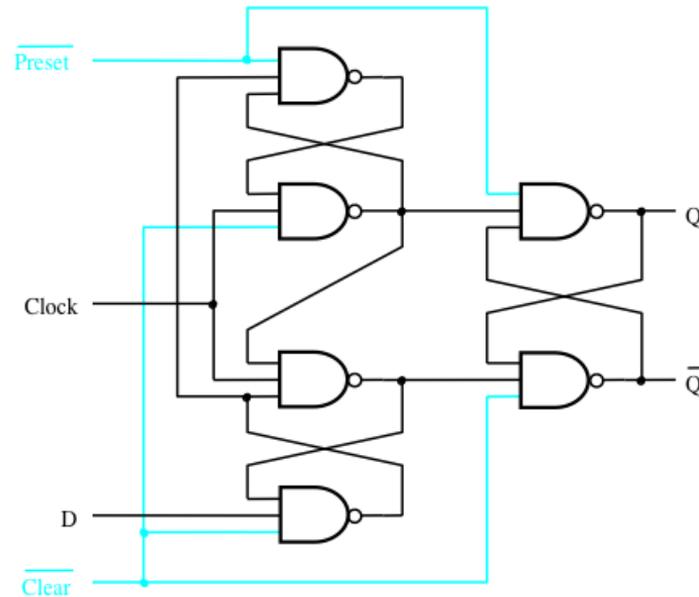
# Edge triggered D flip flop with clear & preset




(a) Circuit

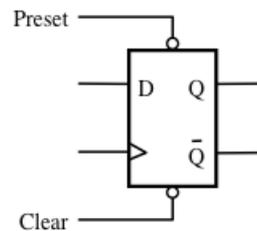

(b) Graphical symbol

Figure 7.14. Positive-edge-triggered D flip-flop with *Clear* and *Preset*.


# T Flip-Flop

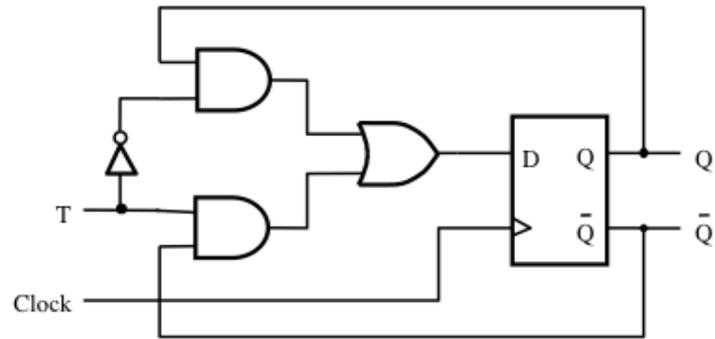


(a) Circuit

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Truth table

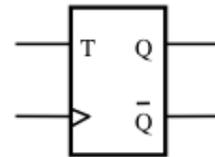

(c) Graphical symbol

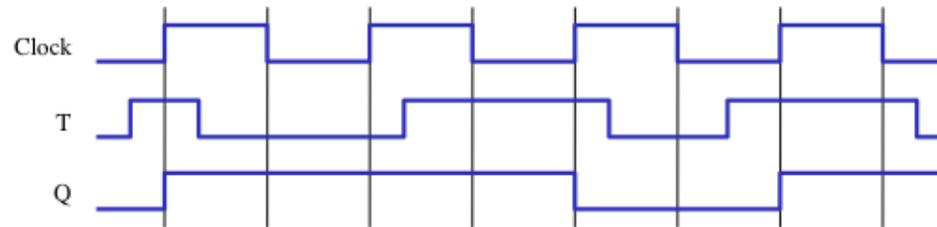


(d) Timing diagram

Figure 7.16. T flip-flop.
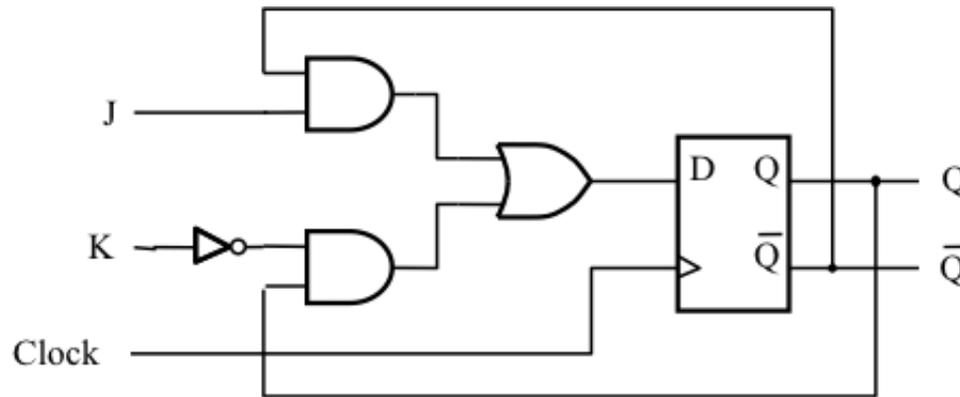
# JK flip flop


- $D = JQ' + K'Q$
- When  $J=S$  and  $K=R$  it will behave like a SR flip-flop



(a) Circuit

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

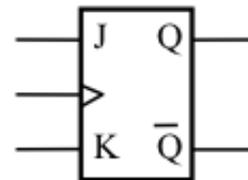

(c) Graphical symbol


# Summary

- Basic latch- a feedback connection of two NOR or NAND gates to store 1-bit information.  $S \gg 1$ ;  $R \gg 0$ .
- Gated latch- a basic latch with a control (clk).  $clk = 0$ : the existing state maintains;  $clk = 1$ : the existing state may change
  - Gated SR latch.  $S \gg 1$ ;  $R \gg 0$ .
  - Gated D latch. The D input forces the state to be the same as D
- Flip-flop- a storage element. Its output state changes only on the edge of clk.
  - Edge-triggered flip-flop
  - Master-slave flip-flop. The master is active in 1<sup>st</sup> half of a clock cycle; The slave active in 2<sup>nd</sup> half.
  - Regardless how many times the D input to the master changes, the slave output can only change at the negative edge of clk.

# Registers

- Register: a set of  $n$  flip-flops used to store  $n$  bits of information
- A common clock is used for all the flip-flops
- A register that provides the ability to shift its contents is called a shift register
- To implement a shift register, it is necessary to use edge-triggered or master-slave flip-flops

# Shift register

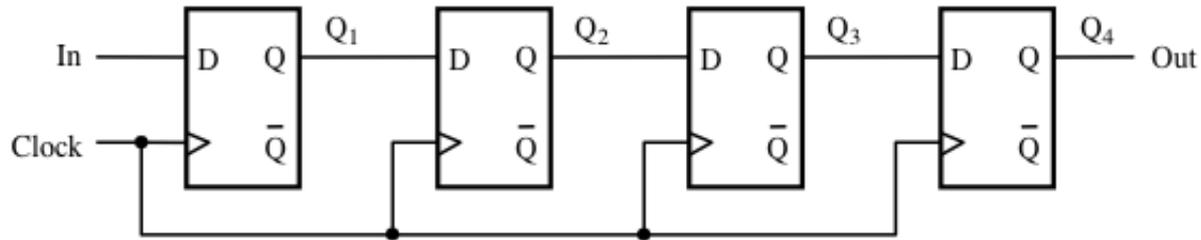

(a) Circuit

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub> = Out
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1

(b) A sample sequence

Figure 7.18. A simple shift register.

- In computer systems it is often necessary to transfer  $n$ -bit data
- Using  $n$  separate wires: parallel transmission
- Using a single wire and performing the transfer one bit at a time in  $n$  consecutive cycles: serial transmission

# Parallel access shift register


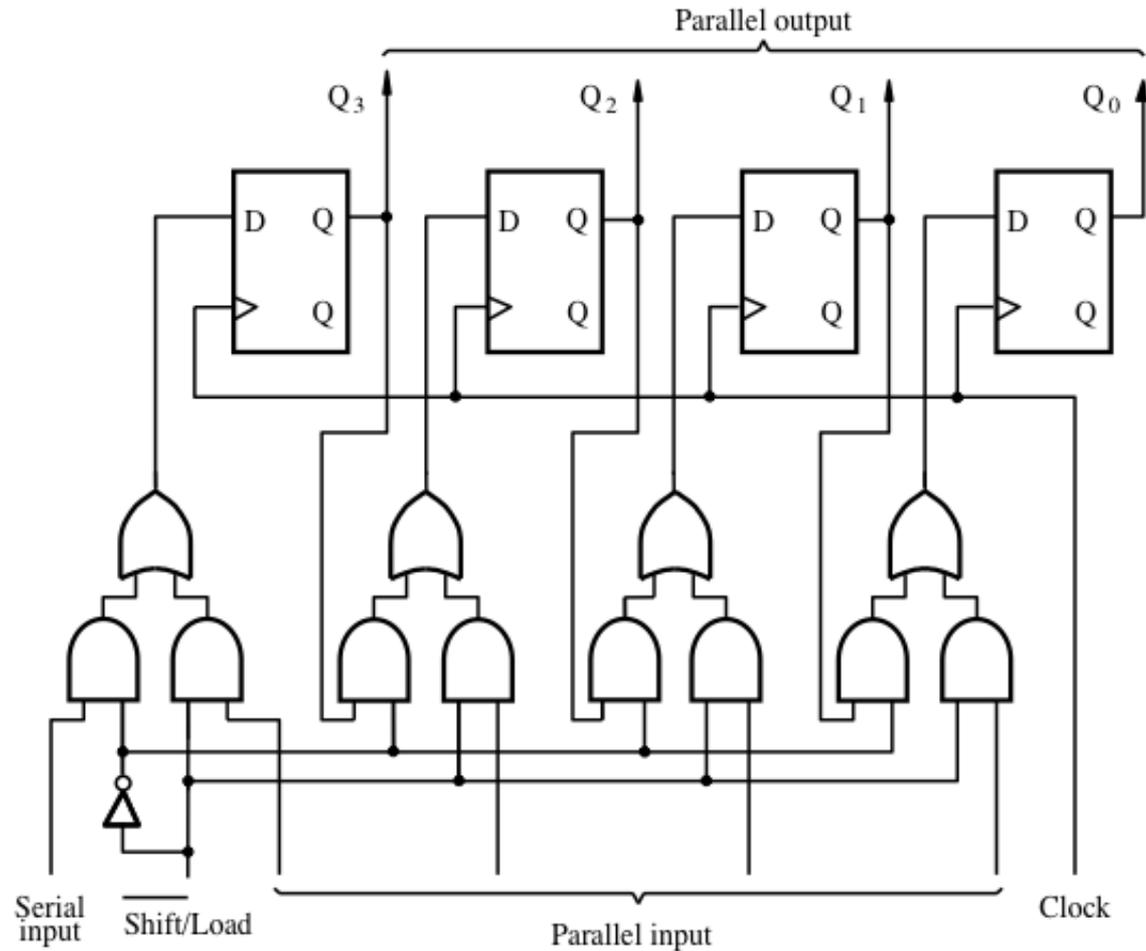


Figure 7.19. Parallel-access shift register.


# Counters

- Counter: a circuit that can increment or decrement a count by 1
- Applications: generating time intervals, count the number of occurrence of an event, ....
- Counters can be build using T and D flip-flops

# Up counter with T flip-flop

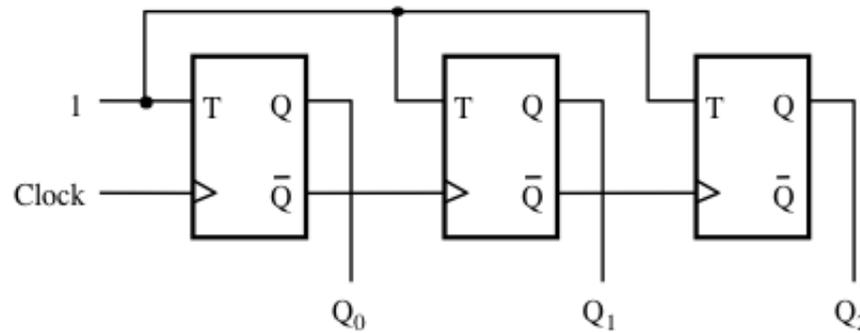


(a) Circuit

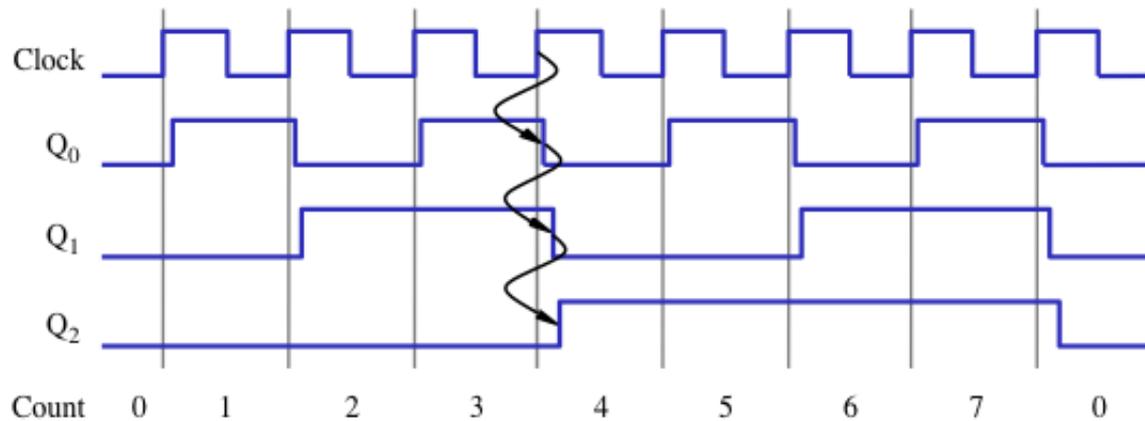

(b) Timing diagram


Figure 7.20. A three-bit up-counter.

# Up counter with T flip-flop

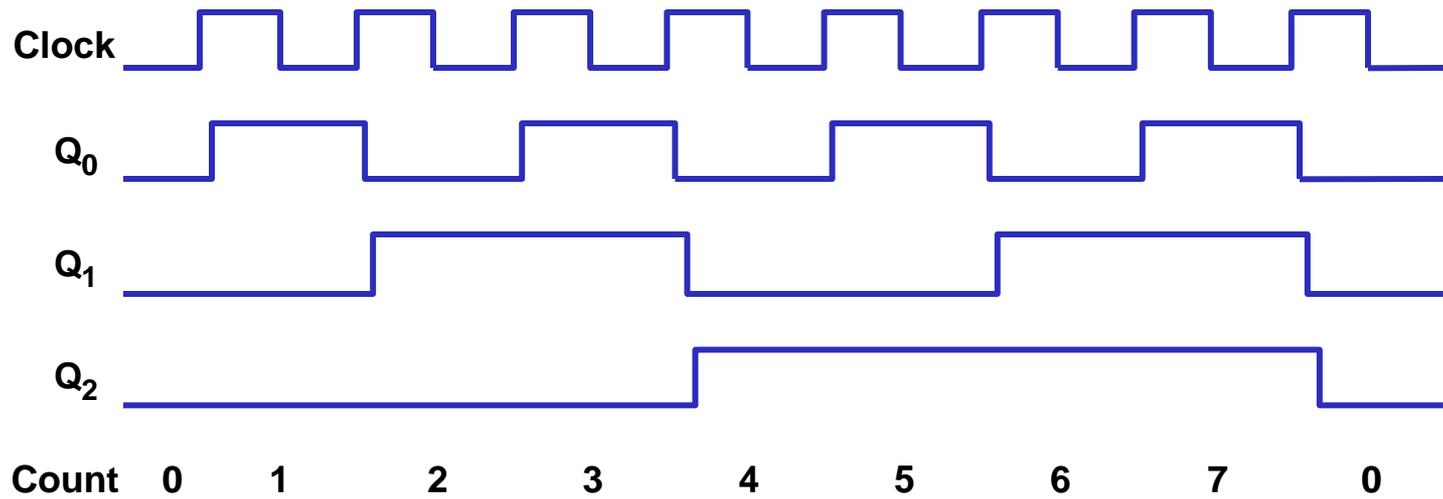


- The counter has three flip flops
- Only the first one is directly connected to the clock
- The other two respond after a delay
- For this reason it is called an asynchronous counter

# Down counter with T flip-flops

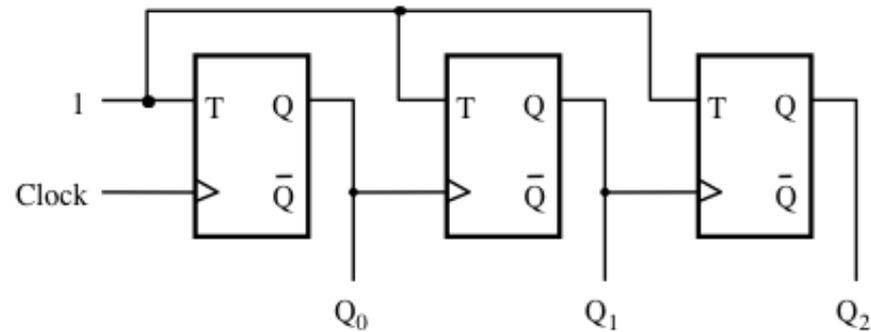

(a) Circuit

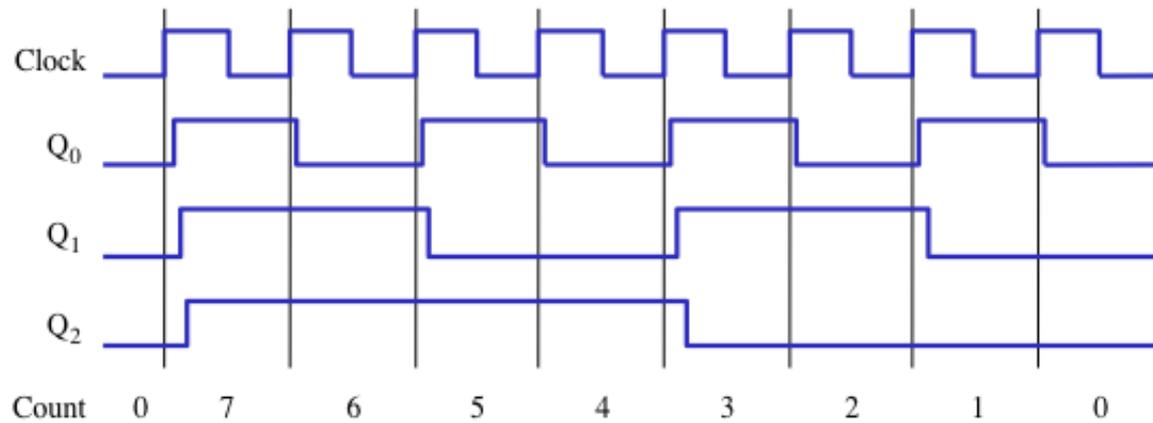


(b) Timing diagram

Figure 7.21. A three-bit down-counter.


# Synchronous counters

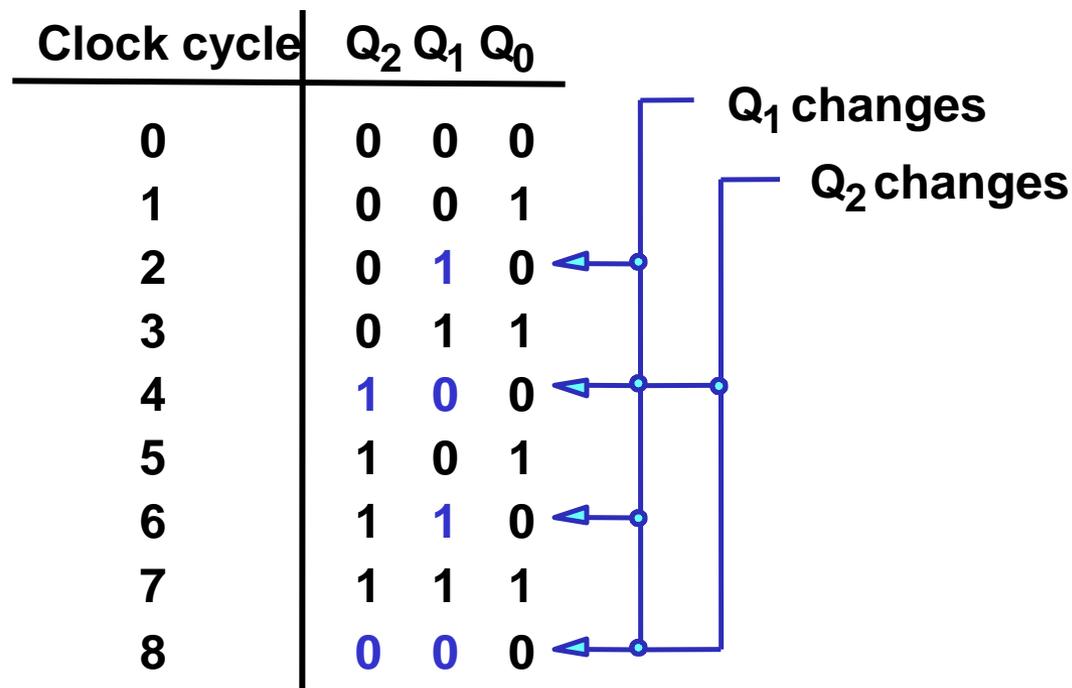- Problem with asynchronous counters: long delays for large number of bits
- Solution: clock all the flip-flops at the same time (synchronous counter)




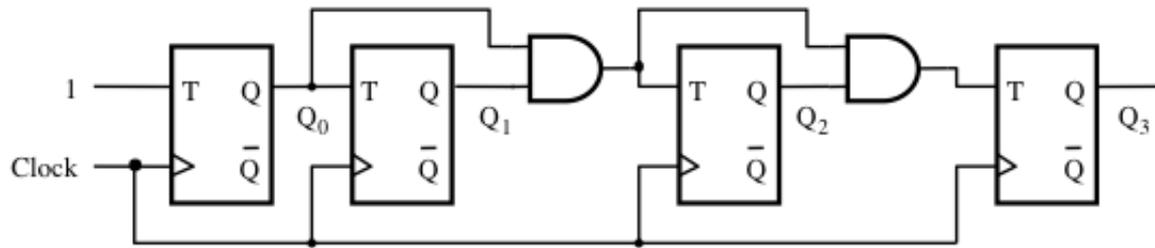- Q0 changes on each clock cycle
- Q1 changes only when Q0=1
- Q2 changes only when Q1=1 and Q0=1

- $T_0=1$ ;
- $T_1=Q_0$
- $T_2=Q_0Q_1$
- $T_3=Q_0Q_1Q_2$



(a) Circuit

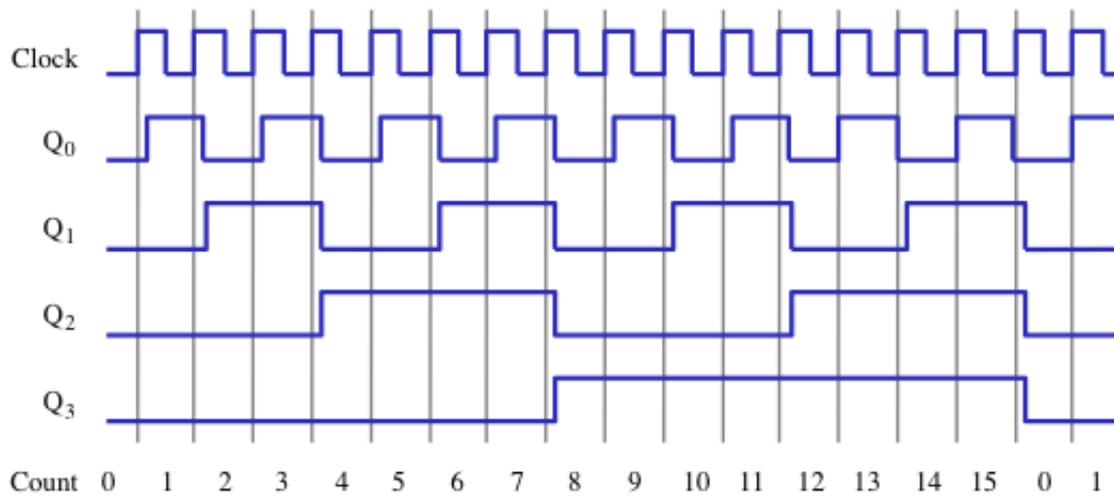

(b) Timing diagram

Figure 7.22. A four-bit synchronous up-counter.

# Enable and clear capability

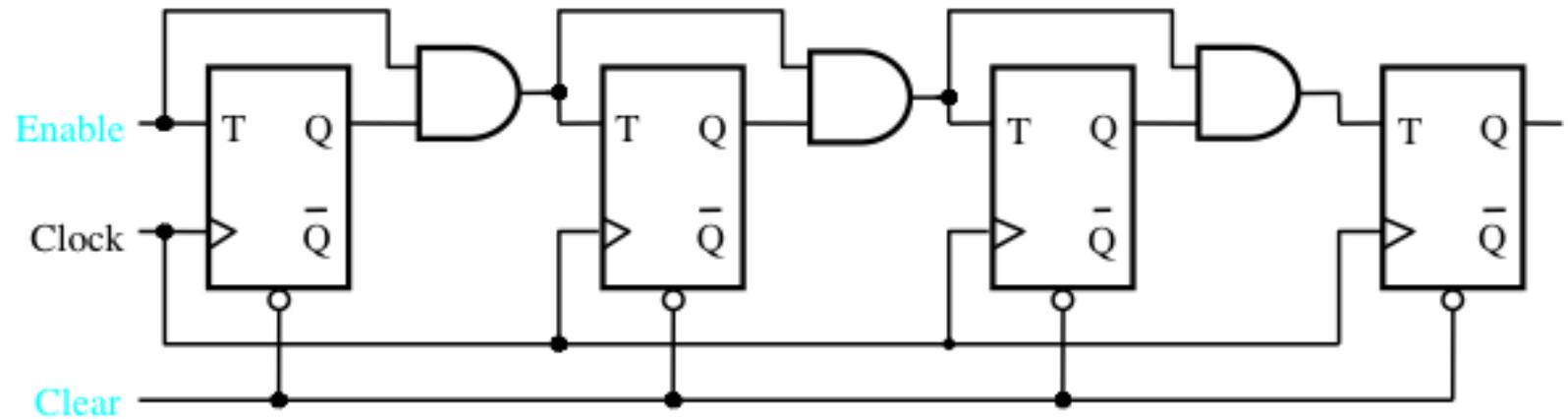


Figure 7.23. Inclusion of Enable and Clear capability.

# Synchronous counter with D flip flop

- Formal method: chapter 8

$$D_0 = Q_0 \oplus Enable$$

$$D_1 = Q_1 \oplus Q_0 \cdot Enable$$

$$D_2 = Q_2 \oplus Q_1 \cdot Q_0 \cdot Enable$$

$$D_3 = Q_3 \oplus Q_2 \cdot Q_1 \cdot Q_0 \cdot Enable$$

# Synchronous Counter with D Flip Flop

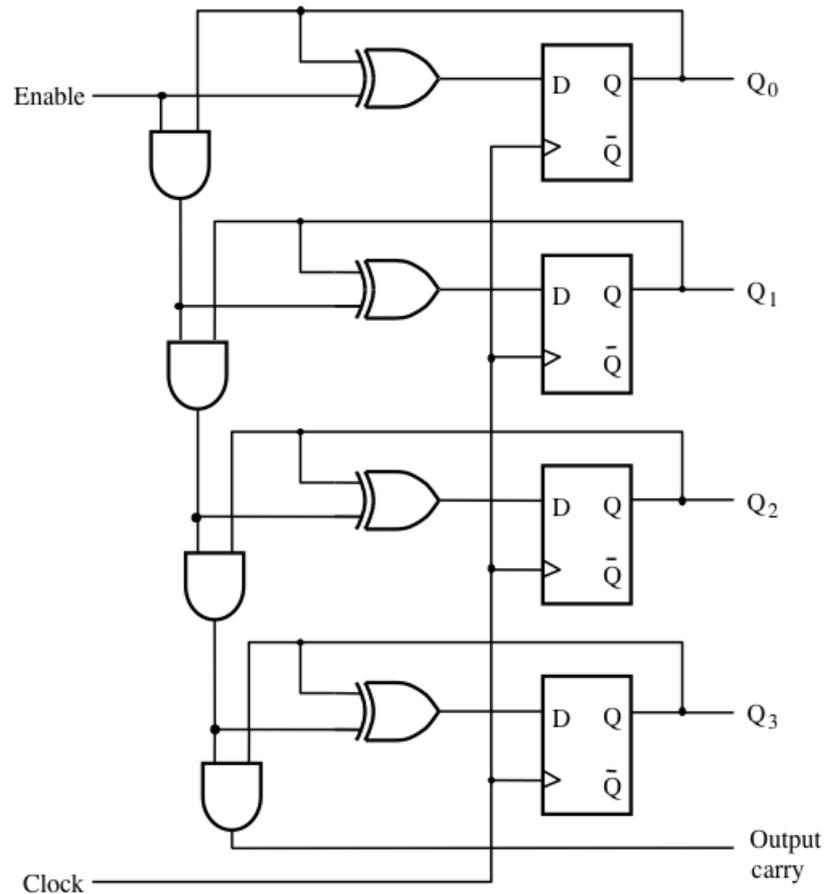


Figure 7.24. A four-bit counter with D flip-flops.


# Counter with parallel load

- Sometimes it is desirable to start the counter with an initial value



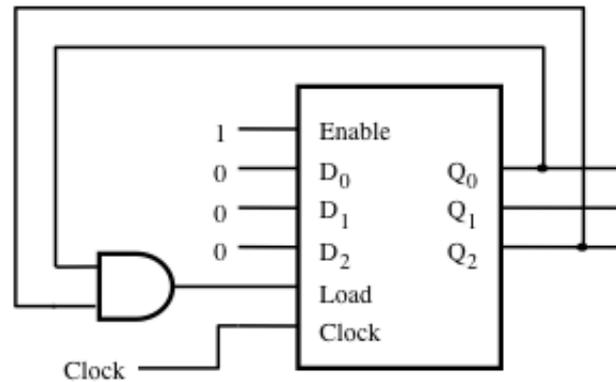
# Reset Synchronization

- How can we design a counter that counts modulo some base that is not a power of 2 (e.g., modulo-6 counter counting 0, 1, 2, 3, 4, 5, 0, 1, ....)
- Detect 5 and then load zero into the counter




(a) Circuit

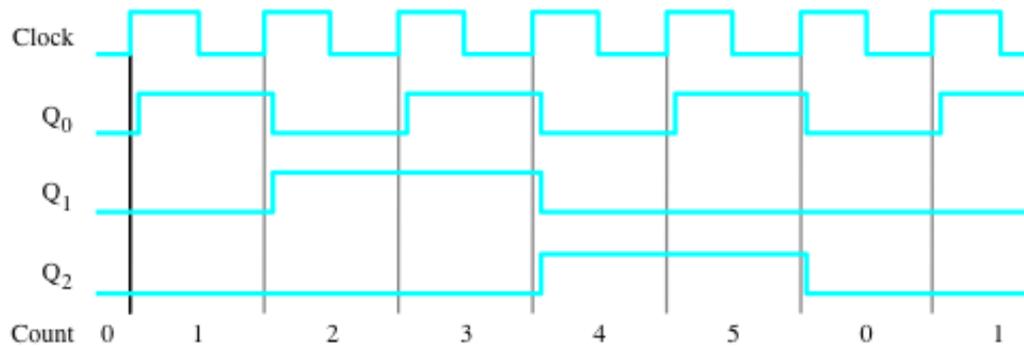


(b) Timing diagram

Figure 7.26. A modulo-6 counter with synchronous reset.

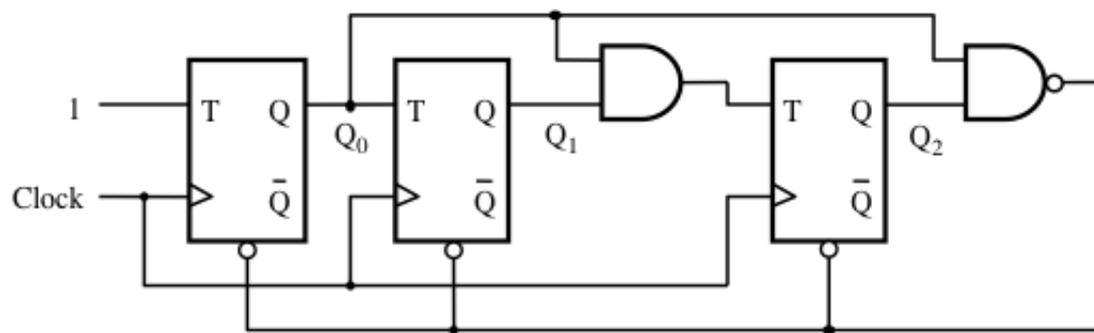

(a) Circuit

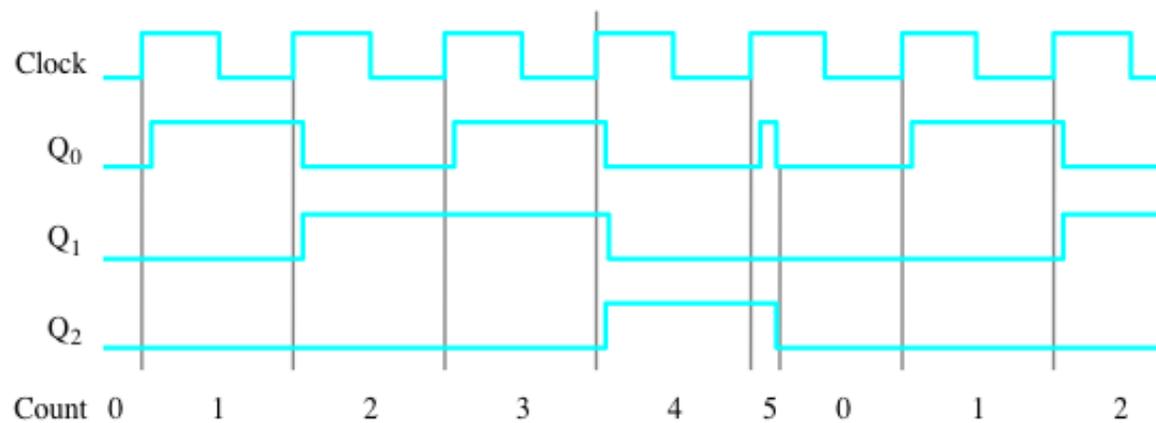

(b) Timing diagram

Figure 7.27. A modulo-6 counter with asynchronous reset.

# BCD counter

- In a BCD counter, the counter should be reset after the count of 9 has been obtained

# BCD Counter


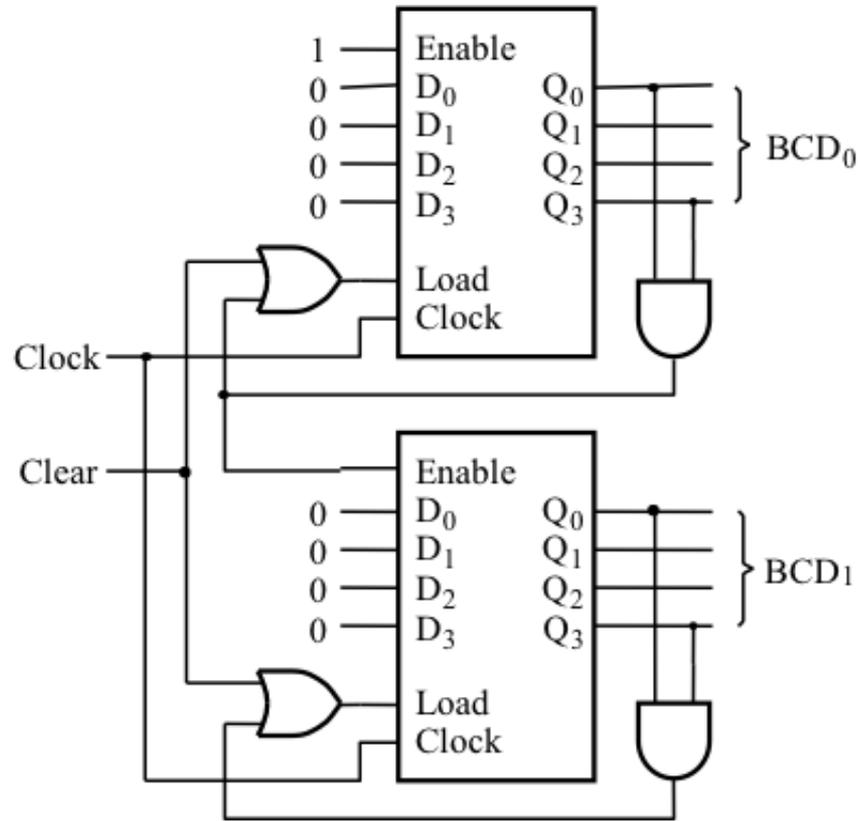


Figure 7.28. A two-digit BCD counter.


# Ring Counter

- In all the previous counters the count is indicated by the state of the flip-flops in the counter
- It is possible to design a counter in which each flip-flop reaches the state of  $Q_i=0$  for exactly one count while for other counts  $Q_i=0$
- This is called a ring counter and it can be built from a shift register

# Ring Counter

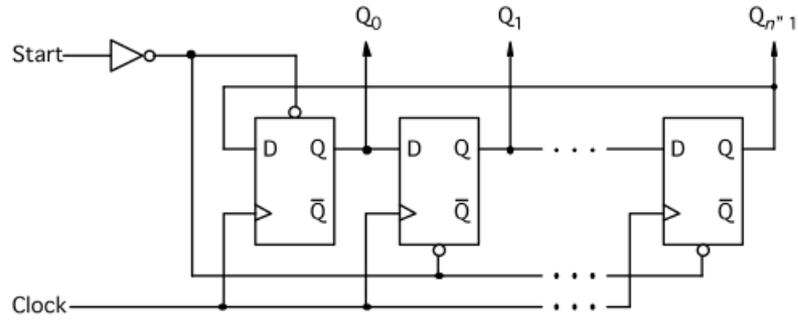

(a) An  $n$ -bit ring counter

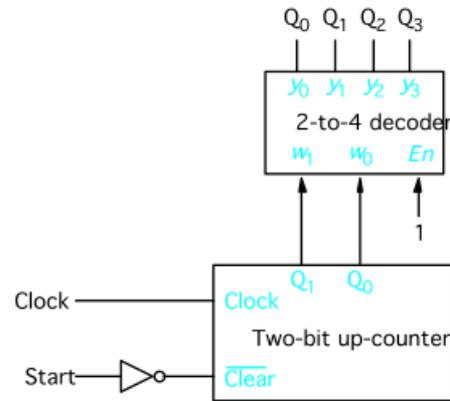

(b) A four-bit ring counter

Figure 7.29. Ring counter.

# Johnson Counter

- If instead of Q output we take the Q' output of the last stage in a ring counter and feed it back to the first stage we get a Johnson counter.
- It counts to a sequence of length  $2n$
- For example for 4-bit the sequence would be: 0000, 0001, 1100, 1110, 1111, 0111, 0011, 0001, 0000.

# Johnson counter

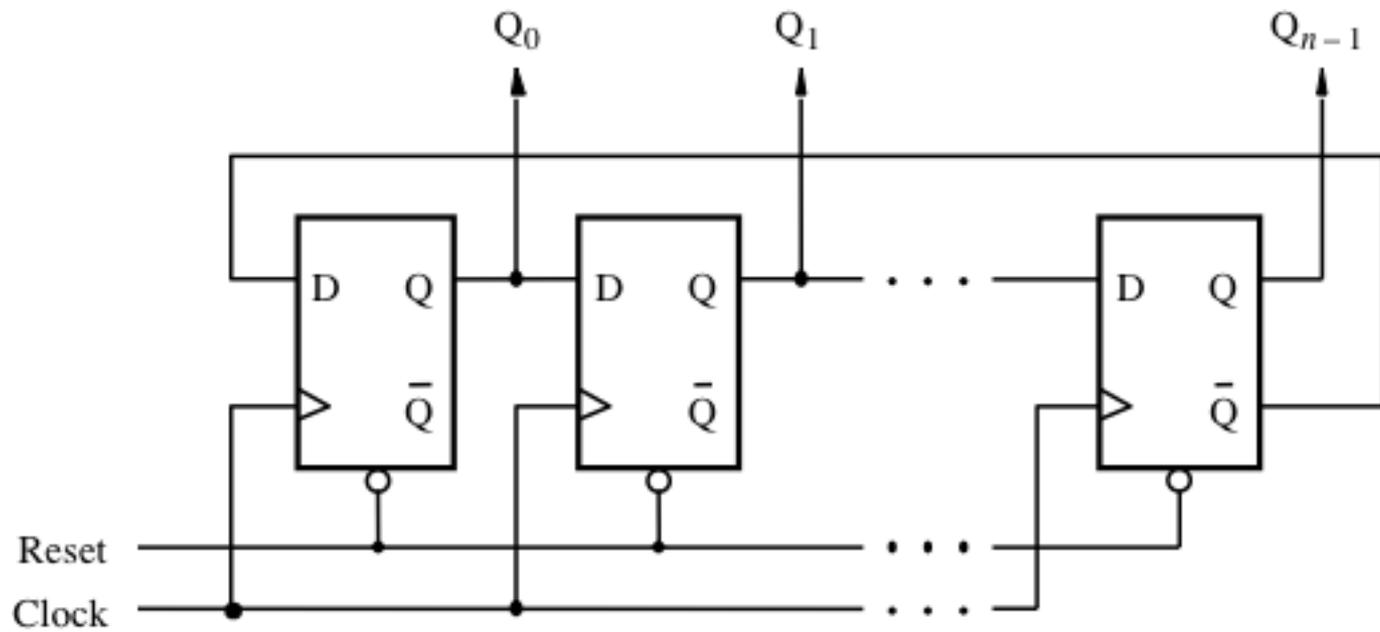


Figure 7.30. Johnson counter.